



Digital Systems and Computer Architecture

Session 2.6


Module 2

Mouli Sankaran

Introduction to Karnaugh map

Session 2.6: Focus

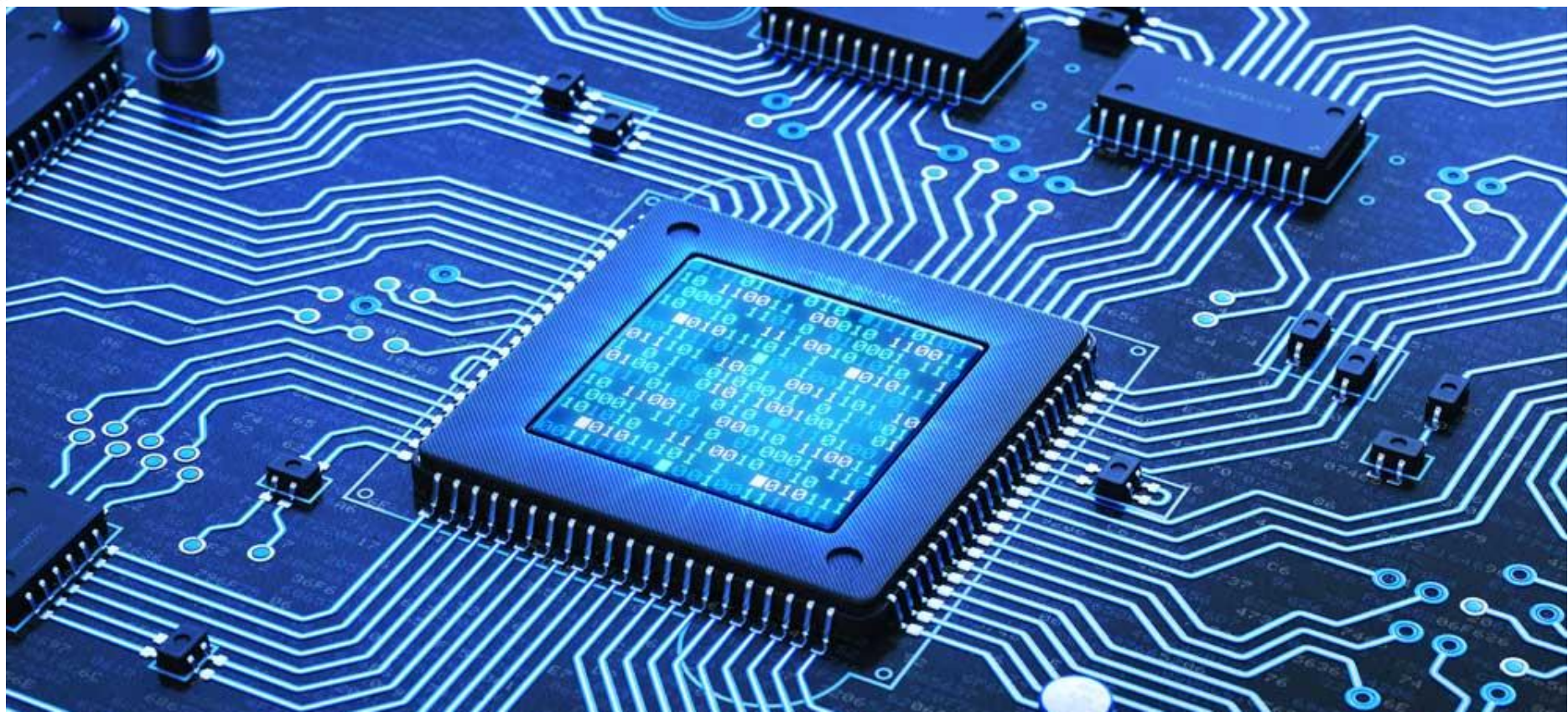- Introduction to Karnaugh map
- Examples
 - SOP form
 - POS form
 - Both SOP and POS
 - Implementation
 - 5-variable K-map
- Don't cares in K-map
 - Example



Karnaugh map Simplification Method

Maurice Karnaugh




Maurice Karnaugh (October 4, 1924 – Nov 8, 2022) is an American physicist and mathematician known for the Karnaugh map used in Boolean algebra.

Karnaugh Map

- The **Karnaugh map**, also known as the **K-map**, is a method to simplify Boolean algebra expressions.
- **Maurice Karnaugh** introduced it in **1953**
- It **reduces** the need for **extensive calculations** by taking advantage of humans' **pattern recognition** capability
- The required Boolean results are **transferred from a truth table onto a two-dimensional grid**
 - Where the cells are **ordered in Gray code**, and
 - **Each cell** position represents **one combination of input conditions**
 - while each **cell value** represents the corresponding **output value**

Sample: Karnaugh Map - corrected

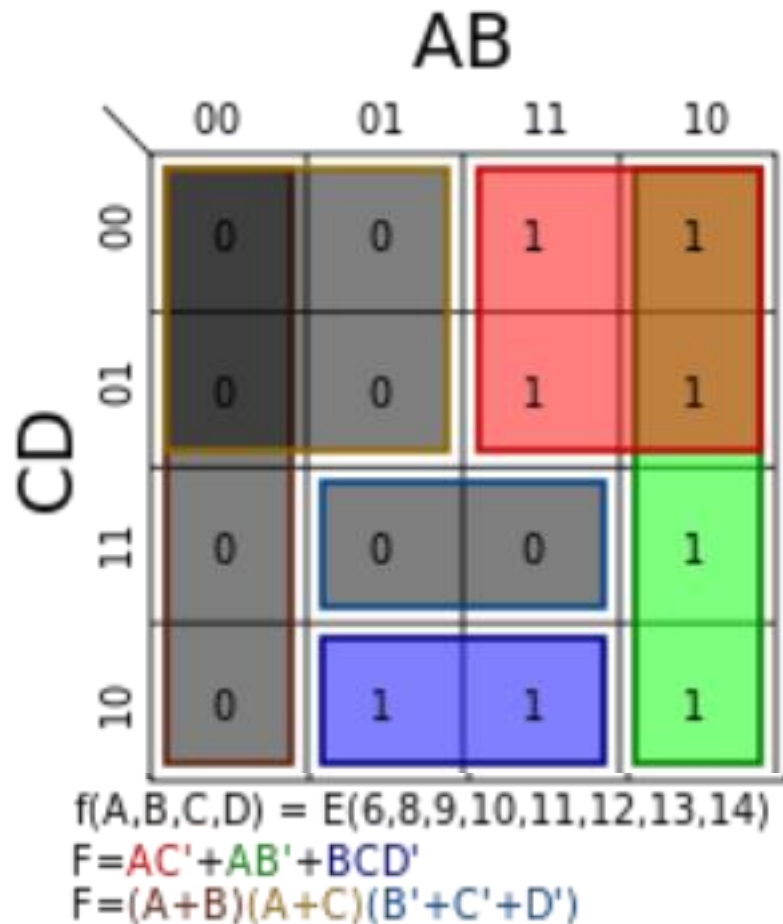

This image actually shows
Two Karnaugh maps:
for the **function f**,
Using **minterms**
(**colored rectangles**)
and
for its **complement f'**,
using **maxterms**
(**gray rectangles**).

Courtesy: Wikipedia

Why Gray Code in K-map?

- The variable combinations in the K-map in the adjacent cells **differ only by one bit**, by ordering them using **Gray codes**
- This helps in simplifying them by combining the adjacent elements if both output **one** (for minterms) or **zero** (for maxterms) since they differ by only one value

Example 1 (SOP)

$$\text{Out} = \overline{A}\overline{B}CD + \overline{A}BCD + ABCD + A\overline{B}CD + AB\overline{C}\overline{D} + AB\overline{C}D + ABC\overline{D}$$

		CD			
		00	01	11	10
A B	00			1	
	01			1	
	11	1	1	1	1
	10			1	

Out = AB + CD


Groups must be a power of 2.

Example 2 (SOP)

$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D}$$

		CD			
		00	01	11	10
AB	00	1			1
	01				
	11				
	10	1			1
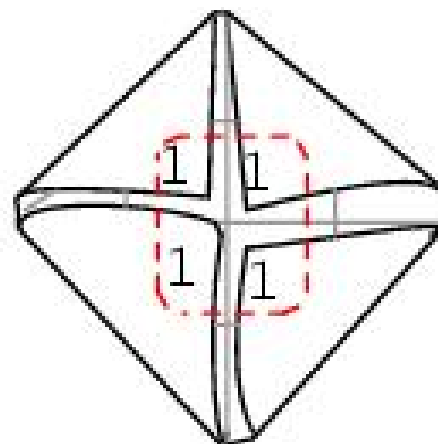
$$\text{Out} = \overline{B}\overline{D}$$



Example 3 (SOP)

$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}CD + A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}D + A\overline{B}C\overline{D} + A\overline{B}CD$$

		CD			
		00	01	11	10
A B	00	1	1	1	1
	01				
	11				
	10	1	1	1	1

$$\text{Out} = \overline{B}$$

Example 4 (SOP)

$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}CD + B\overline{C}\overline{D} + B\overline{C}D + A\overline{B}\overline{C}\overline{D} + A\overline{B}D + A\overline{B}C\overline{D}$$

A \ B \ CD	00	01	11	10
00	1	1	1	1
01	1			1
11	1			1
10	1	1	1	1

A \ B \ CD	00	01	11	10
00	1	1	1	1
01	1			1
11	1			1
10	1	1	1	1

Out = $\overline{B} + \overline{D}$

Example 5 (SOP)

$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + A\overline{B}\overline{C}\overline{D} + ABCD$$

		CD			
A	B	00	01	11	10
	00	1			1
	01				
	11			1	
	10	1			

$$\text{Out} = \overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{D} + ABCD$$

Example 6 (SOP)

$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}D \\ + ABCD + ABC\overline{D} + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D}$$

A \ B \ CD	00	01	11	10
00	1	1		
01		1	1	
11			1	1
10	1			1

A \ B \ CD	00	01	11	10
00	1	1		
01		1	1	
11			1	1
10	1			1

$$\text{Out} = \overline{B}\overline{C}\overline{D} + \overline{A}\overline{C}D + BCD + A\overline{C}\overline{D}$$

$$\text{Out} = \overline{A}\overline{B}\overline{C} + \overline{A}BD + ABC + A\overline{B}\overline{D}$$

Example 7 (SOP)

$$\begin{aligned} \text{Out} = & \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} \\ & + \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}BC\overline{D} \\ & + AB\overline{C}\overline{D} + AB\overline{C}D + ABC\overline{D} \end{aligned}$$

A \ B	CD			
	00	01	11	10
00	1	1	1	
01	1	1	1	
11	1	1	1	
10				

A \ B	CD			
	00	01	11	10
00	1	1	1	
01	1	1	1	
11	1	1	1	
10				

A \ B	CD			
	00	01	11	10
00	1	1	1	
01	1	1	1	
11	1	1	1	
10				

$$\text{Out} = \overline{A}\overline{C} + \overline{A}D + B\overline{C} + BD$$

Example 8 (SOP)

$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}D + ABC\overline{D} + ABCD + A\overline{B}C\overline{D} + A\overline{B}CD$$

		CD			
		00	01	11	10
A \ B	00	1		1	
	01	1		1	
	11	1	1	1	
	10	1		1	

$$\text{Out} = \overline{C}\overline{D} + CD + A\overline{B}\overline{C}$$

		CD			
		00	01	11	10
A \ B	00	1		1	
	01	1		1	
	11	1	1	1	
	10	1		1	

$$\text{Out} = \overline{C}\overline{D} + CD + ABD$$

Example 9 (SOP)

$$\text{Out} = \bar{C} + ABCD$$

		CD			
A	B	00	01	11	10
		00	01	11	10
00		1	1		
01		1	1		
11		1	1	1	
10		1	1		

$$\text{Out} = \bar{C} + ABD$$

Simplification by Boolean Algebra

$$\text{Out} = \bar{C} + ABCD$$

Applying rule $A + \bar{A}B = A + B$ to the $\bar{C} + ABCD$ term

$$\text{Out} = \bar{C} + ABD$$

SOP and POS Forms

$AB \backslash CD$		C			
		00	01	11	10
00	m_0	1	1	m_3 0	m_2 1
	m_4	0	1	m_7 0	m_6 0
01	m_{12}	0	0	m_{15} 0	m_{14} 0
	m_8	1	1	m_{11} 0	m_{10} 1

SOP

$$F = B'D' + B'C' + A'C'D$$

Combining 0 terms yields:

$$F' = AB + CD + BD'$$

Applying DeMorgan's theorem

Complement of F' is F

POS

$$F = (A' + B')(C' + D')(B' + D)$$


Example 1 (POS)

$$\text{Out} = (A + B + C)$$

$$\text{Maxterm} = A + B + C$$

$$\text{Numeric} = 1 \ 1 \ 1$$

$$\text{Complement} = 0 \ 0 \ 0$$

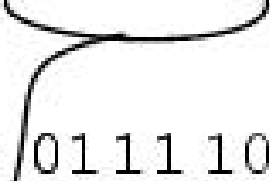

A \ BC				
	00	01	11	10
0	0	1	1	1
1	1	1	1	1

Example 2 (POS)

$$\text{Out} = (\bar{A} + \bar{B} + \bar{C})$$

$$\text{Maxterm} = \bar{A} + \bar{B} + \bar{C}$$

$$\text{Numeric} = 0 \ 0 \ 0$$

$$\text{Complement} = 1 \ 1 \ 1$$

A \ BC	00	01	11	10
0	1	1	1	1
1	1	1	0	1


Example 3 (POS) ... contd in the next slide

$$\text{Out} = (A + B + C) (A + B + \overline{C})$$

$$\text{Maxterm} = (A + B + C) \quad \text{Maxterm} = (A + B + \overline{C})$$

$$\text{Numeric} = 1 \ 1 \ 1 \quad \text{Numeric} = 1 \ 1 \ 0$$

$$\text{Complement} = 0 \ 0 \ 0 \quad \text{Complement} = 0 \ 0 \ 1$$



A \ BC	00	01	11	10
0	0	0	1	1
1	1	1	1	1

Example 3 (POS) - contd

$$\text{Out} = (A + B + C) (A + B + \overline{C})$$

A \ BC				
	00	01	11	10
0	0	0	1	1
1	1	1	1	1

$$A \ B \ C = 0 \ 0 \ X$$

$$\text{Complement} = 1 \ 1 \ X$$

$$\text{Sum-term} = (A + B)$$

$$\text{Out} = (A + B)$$

Quiz 1

Simplify the Boolean expression using K-map

$$\text{Out} = (A+B+C+\bar{D})(A+B+\bar{C}+D)(A+\bar{B}+C+\bar{D})(A+\bar{B}+\bar{C}+D) \\ (\bar{A}+\bar{B}+\bar{C}+D)(\bar{A}+B+C+\bar{D})(\bar{A}+B+\bar{C}+D)$$

$$\text{Out} = (A+B+C+\bar{D})(A+B+\bar{C}+D)(A+\bar{B}+C+\bar{D})(A+\bar{B}+\bar{C}+D) \\ (\bar{A}+\bar{B}+\bar{C}+D)(\bar{A}+B+C+\bar{D})(\bar{A}+B+\bar{C}+D)$$

		CD			
		00	01	11	10
AB	00		0		0
	01		0		0
	11				0
	10		0		0

Quiz 1: Solution

		input				complement	Sum-term	
A B	CD	00	01	11	10			
00			0		0	$ABCD = X001$	$> X110 >$	$(B + C + \bar{D})$
01			0		0	$ABCD = 0X01$	$> 1X10 >$	$(A + C + \bar{D})$
11					0	$ABCD = XX10$	$> XX01 >$	$(\bar{C} + D)$
10			0		0			

Out= $(B + C + \bar{D}) (A + C + \bar{D}) (\bar{C} + D)$

Quiz 2:

Simplify the **Product-Of-Sums** Boolean expression below, providing a **result** in **SOP** form

$$\text{Out} = (A + B + C + \bar{D}) (A + B + \bar{C} + D) (A + \bar{B} + C + \bar{D}) (A + \bar{B} + \bar{C} + D) \\ (\bar{A} + \bar{B} + \bar{C} + D) (\bar{A} + B + C + \bar{D}) (\bar{A} + B + \bar{C} + D)$$

		CD			
		00	01	11	10
A B	00		0		0
	01		0		0
	11				0
	10		0		0



		CD			
		00	01	11	10
A B	00	1	0	1	0
	01	1	0	1	0
	11	1	1	1	0
	10	1	0	1	0

Quiz 2: Solution

Simplify the Product-Of-Sums Boolean expression below, providing a **result** in **SOP** form

$$\text{Out} = (A + B + C + \bar{D}) (A + B + \bar{C} + D) (A + \bar{B} + C + \bar{D}) (A + \bar{B} + \bar{C} + D) \\ (\bar{A} + \bar{B} + \bar{C} + D) (\bar{A} + B + C + \bar{D}) (\bar{A} + B + \bar{C} + D)$$

		CD			
		00	01	11	10
AB	00	1	0	1	0
	01	1	0	1	0
	11	1	1	1	0
	10	1	0	1	0

$$\text{Out} = \bar{C}\bar{D} + CD + ABD$$

Same Example: Both SOP and POS

$$\text{Out} = (A + B + C + \bar{D}) (A + B + \bar{C} + D) (A + \bar{B} + C + \bar{D}) (A + \bar{B} + \bar{C} + D) \\ (\bar{A} + \bar{B} + \bar{C} + D) (\bar{A} + B + C + \bar{D}) (\bar{A} + B + \bar{C} + D)$$

A \ B		CD			
		00	01	11	10
00			0		0
01			0		0
11					0
10			0		0


A \ B		CD			
		00	01	11	10
00		1		1	
01		1		1	
11		1	1	1	
10		1		1	

$$\text{Out} = \bar{C}\bar{D} + CD + ABD$$


$$\text{Out} = (B + C + \bar{D}) (A + C + \bar{D}) (\bar{C} + D)$$

Implementation
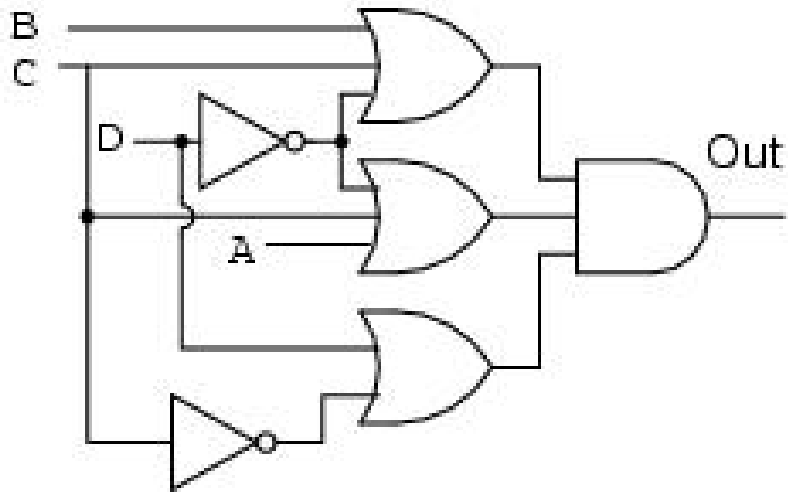
$$\text{Out} = (B + C + \bar{D})(A + C + \bar{D})(\bar{C} + D)$$



$$\text{Out} = \bar{C}\bar{D} + CD + ABD$$

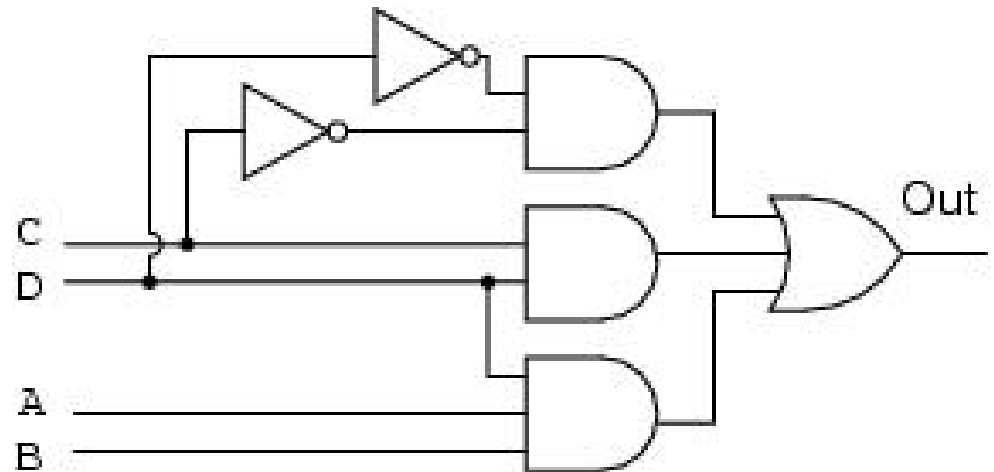

Session 2.6: Summary

- Introduction to Karnaugh map
- Examples
 - SOP form
 - POS form
 - Both SOP and POS
 - Implementation