



Digital Systems and Computer Architecture

Session 2.2


Module 2

Mouli Sankaran

Logic Gates and Binary Adders and Subtractors

Session 2.2: Focus

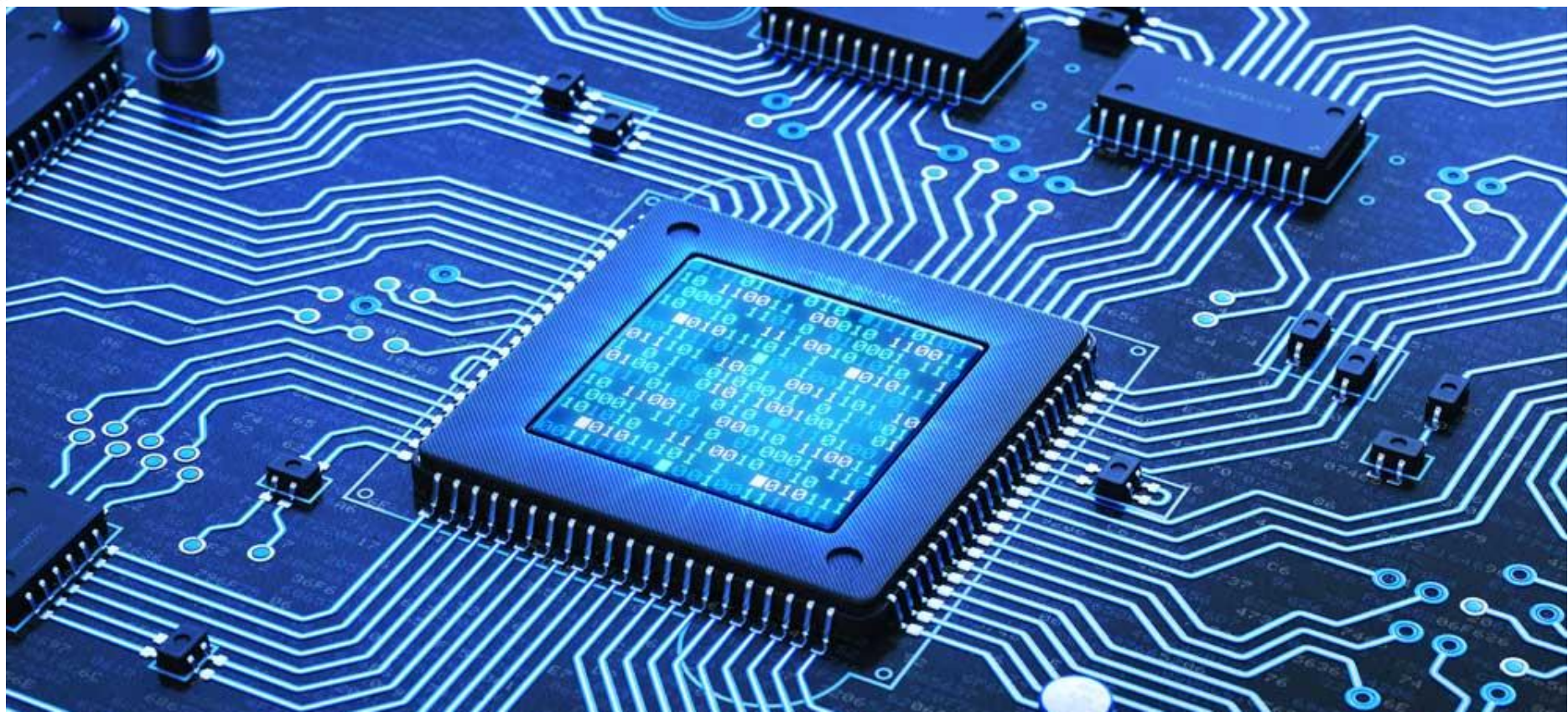
- Logic Gates
- AND, OR, NOT
- NAND and NOR
- XOR and Exclusive-NOR
- Logic Gates - ICs
- Binary Addition
 - Half and Full Adder Circuits
- Binary Subtraction
 - Half and Full Subtractor Circuits
- 7-Segment Display



Logic Gates

Logic Signals

 - The logic signals (**0 and 1**) with which logic gates are driven are shown here
- The voltage levels have consistently come down due to **low power** requirements from **3V** to **less than 1V**




AND, OR, NOT Gates




(a) Two-input AND gate



(b) Two-input OR gate

 

(c) NOT gate or inverter

 


Truth Tables of Logical Operations

AND			OR			NOT	
x	y	$x \cdot y$	x	y	$x + y$	x	x'
0	0	0	0	0	0	0	1
0	1	0	0	1	1	1	0
1	0	0	1	0	1		
1	1	1	1	1	1		

Quiz 1: Draw the Output signals

Inputs to the
gates

 


Outputs of
the gates

x AND y


x OR y

NOT x

Quiz 2: Give Truth Table

 

(a) Three-input AND gate

 

(b) Four-input OR gate

Answer for (a):


A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Answer for (b):


If any one input is 1,
the output (**G**) will be one

G is zero only when all
A, B, C, D are zeros

Quiz 3: Draw the Output waveform

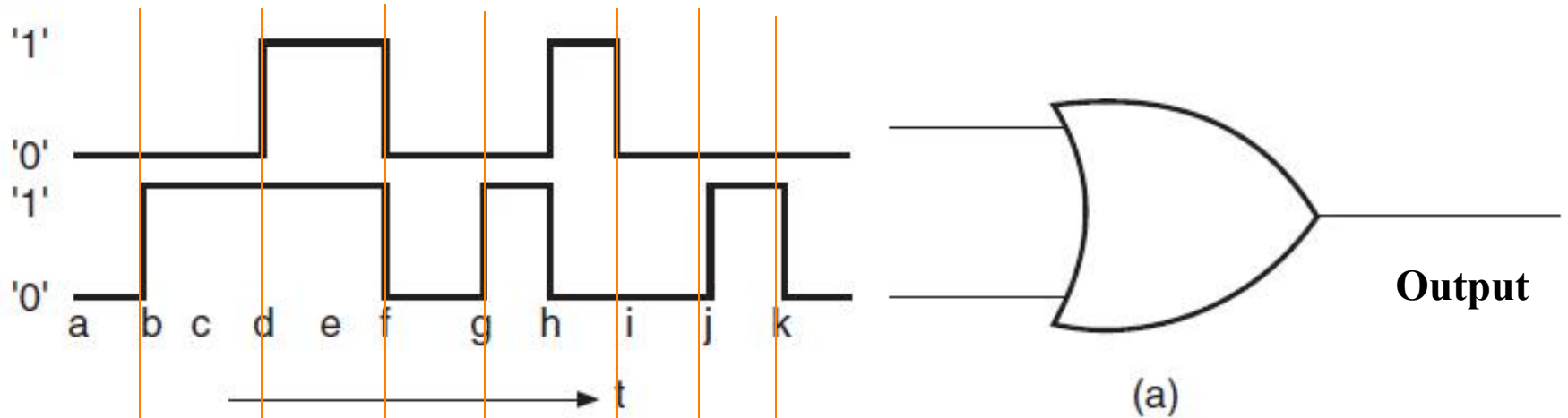


Answer:

 


Output

Quiz 4: What are the Outputs?


Answers:

 

Always One

 


Always Zero

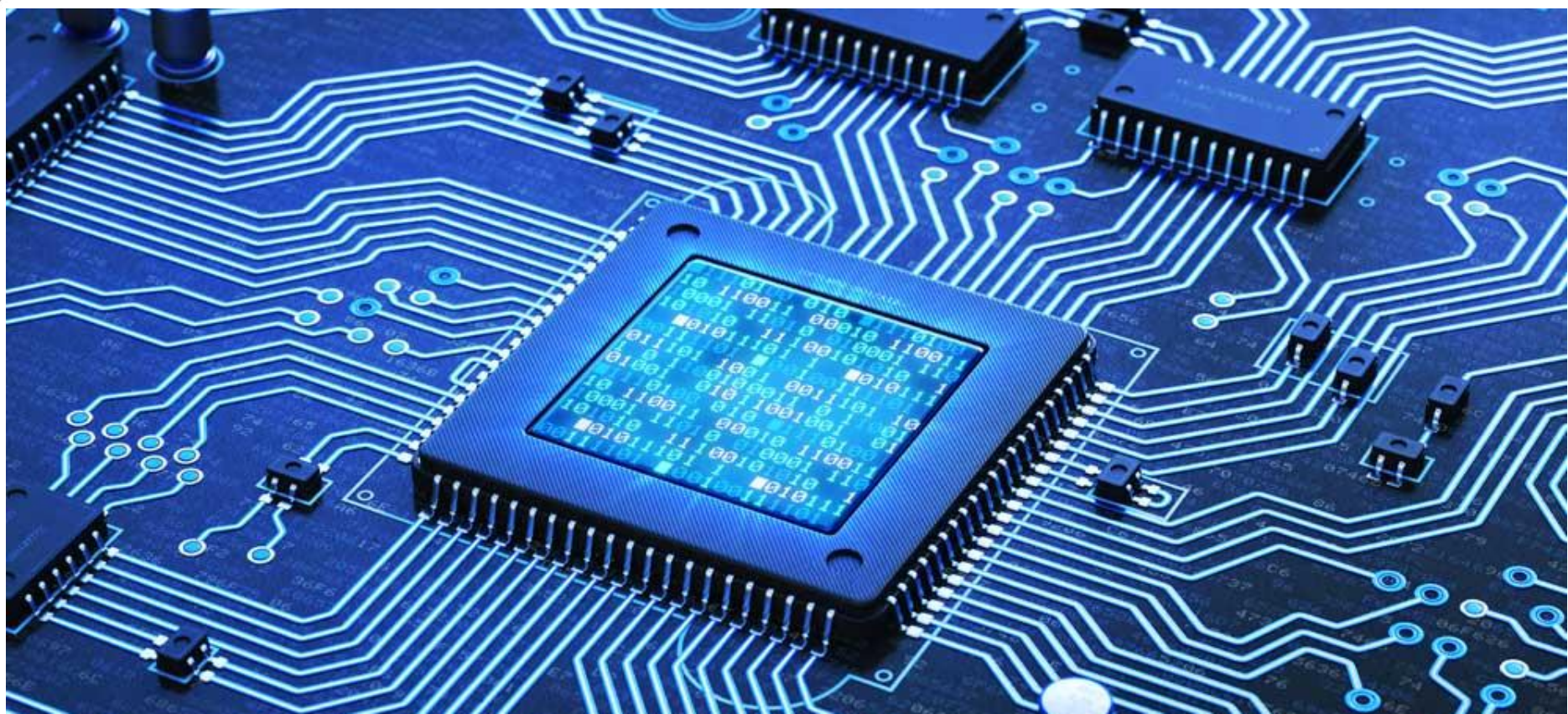

NAND and NOR Gates

NAND Gates

 

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


$$Y = \overline{A.B}$$



Can also be written as:


$$Y = \overline{A} \overline{B}$$

NAND Gate with more than two inputs:

 


$$Y = \overline{(A.B.C)}$$

NOR Gates

 


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

$$Y = \overline{A+B}$$

 


3-input NOR Gate :

TRUTH TABLE

 


INPUTS			OUTPUT
W	X	Y	Z
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$$Y = \overline{(A+B+C)}$$

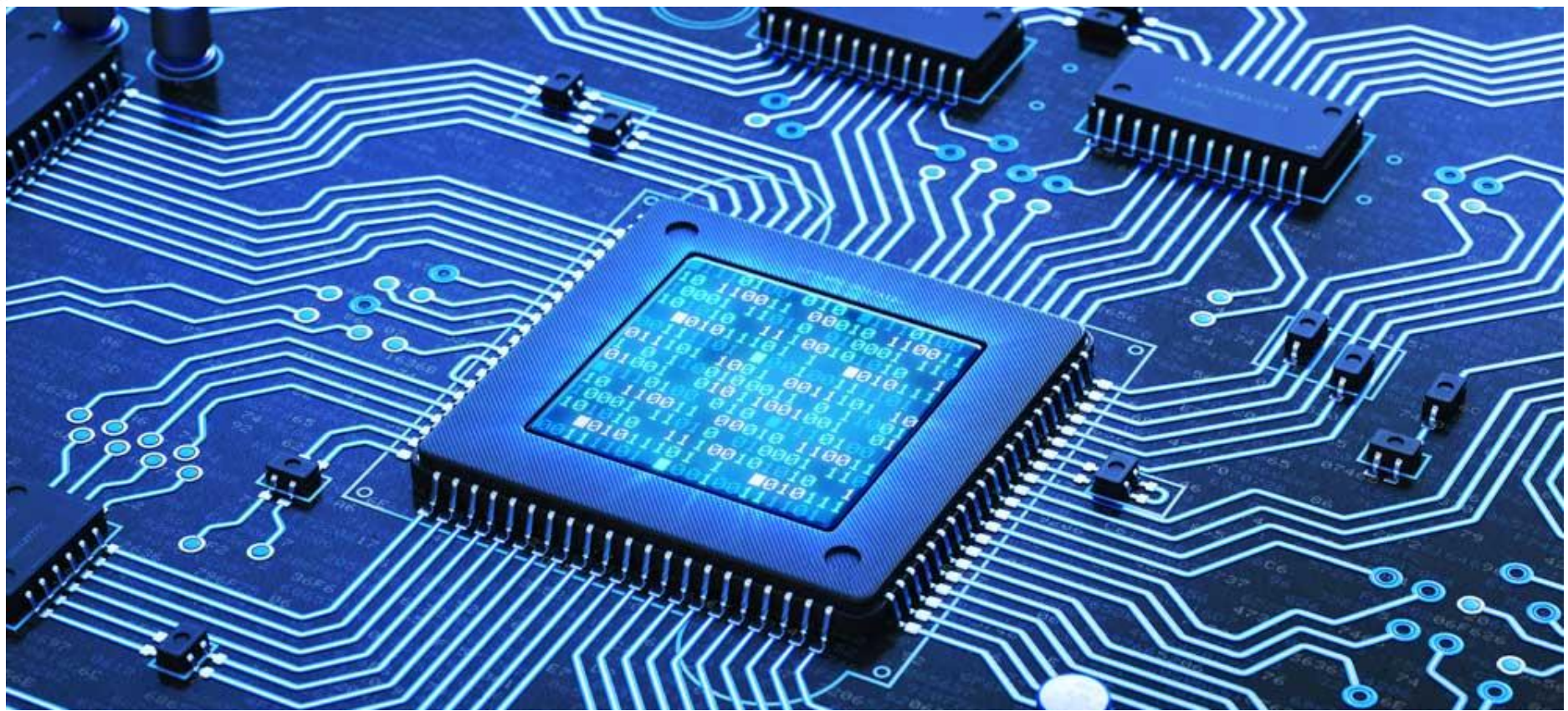

XOR Gate


XOR Gate

 

Truth Table of XOR Gate:



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

XOR Gates

 


- **XOR** gate is sometimes referred to as “**anything but not all**”
- XOR gate is enabled only when there are **odd number** of digital **1s**
- Therefore, an XOR gate can be viewed as an **odd bits check circuit**

Multiple input XOR Gate

  

1. **Output is 1 when only when either there are one or three 1s as inputs**
2. **Output is one when there are odd 1s as inputs**

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

 

Exclusive-NOR Gates


Exclusive-NOR Gates



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

$$Y = \overline{A \oplus B}$$


3-input Exclusive-NOR Gate :

 

Inputs			outputs
W	X	Y	$Q = \overline{A \oplus B \oplus C}$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0


$$Q = \overline{A \oplus B \oplus C}$$

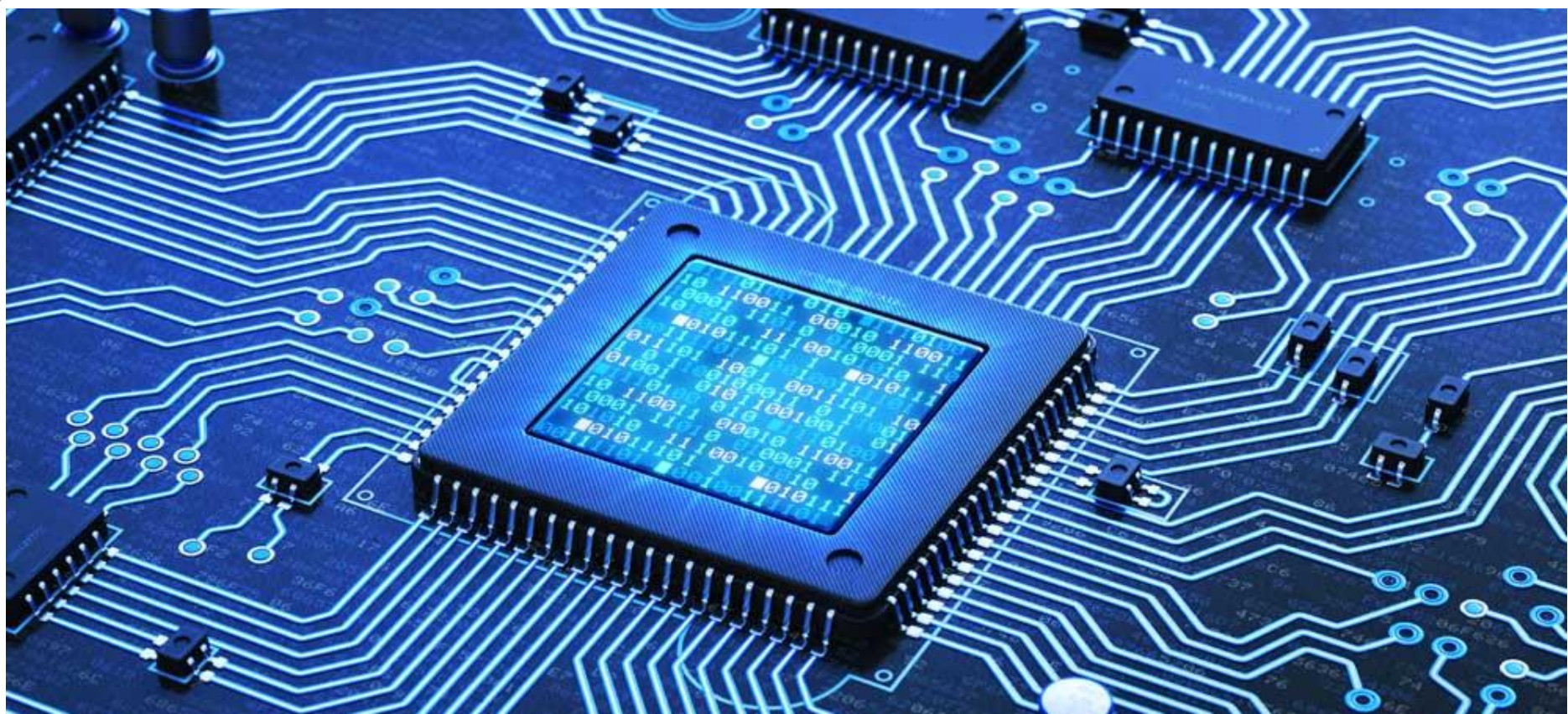This is an **Even function**.
Output is 1 when there
 are **even number**
 of **1s as inputs**




Logic Gates ICs

74LS Series ICs

 


Pin Numbers

 


LS: Low-power Schottky family


Some 74LS Series ICs

 


7400

 


7402

 

7404

 

7408

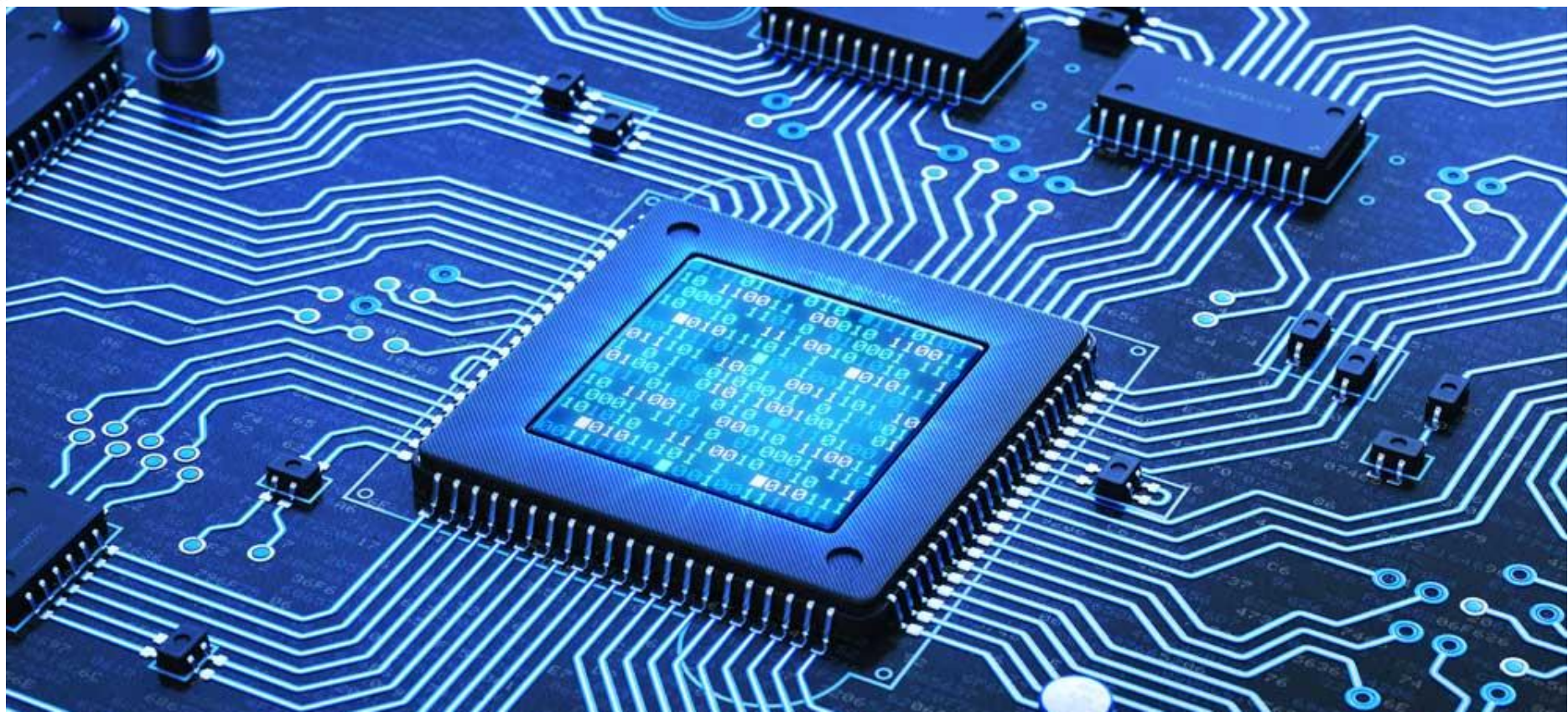

Binary Addition



Basic Rules of Binary Addition (Half Adder)

$$A + B = \text{Sum (S)}$$

1. $0 + 0 = 0.$
 2. $0 + 1 = 1.$
 3. $1 + 0 = 1.$
 4. $1 + 1 = 0$ with a carry of '1' to the next more significant bit.
- } **Carry is zero**


Inputs		Outputs	
A	B	S	C
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1

Truth table

  

3-bit Binary Addition (Full Adder)

A	B	Carry-in (C_{in})	Sum	Carry-out (C_o)	A	B	Carry-in (C_{in})	Sum	Carry-out (C_o)
0	0	0	0	0	1	0	0	1	0
0	0	1	1	0	1	0	1	0	1
0	1	0	1	0	1	1	0	0	1
0	1	1	0	1	1	1	1	1	1

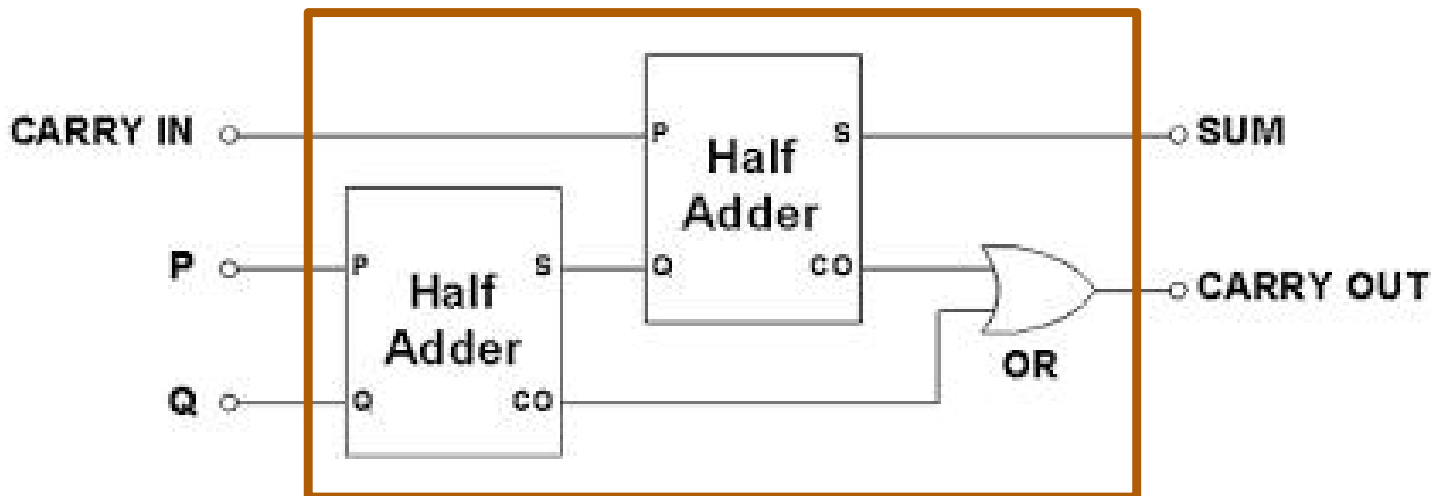

Larger-bit Binary Addition


- Consider **32 bit adders** are used to add **two 128 bit numbers** $(A_3 A_2 A_1 A_0)$ and $(B_3 B_2 B_1 B_0)$ **Note:** Consider each of them are 32-bit numbers

$$\begin{array}{r}
 1. \quad \begin{array}{cccc} & & (C_0) & \\ A_3 & A_2 & A_1 & A_0 \\ B_3 & B_2 & B_1 & B_0 \end{array} \\
 \hline
 \phantom{\begin{array}{cccc} & & (C_0) & \\ A_3 & A_2 & A_1 & A_0 \\ B_3 & B_2 & B_1 & B_0 \end{array}} S_0 \\
 \hline
 \end{array}$$

$$\begin{array}{r}
 2. \quad \begin{array}{cccc} & & (C_1) & (C_0) \\ A_3 & A_2 & A_1 & A_0 \\ B_3 & B_2 & B_1 & B_0 \end{array} \\
 \hline
 \phantom{\begin{array}{cccc} & & (C_1) & (C_0) \\ A_3 & A_2 & A_1 & A_0 \\ B_3 & B_2 & B_1 & B_0 \end{array}} S_1 \quad S_0 \\
 \hline
 \end{array}$$

$$\begin{array}{r}
 3. \quad \begin{array}{cccc} (C_2) & (C_1) & (C_0) & \\ A_3 & A_2 & A_1 & A_0 \\ B_3 & B_2 & B_1 & B_0 \end{array} \\
 \hline
 \phantom{\begin{array}{cccc} (C_2) & (C_1) & (C_0) & \\ A_3 & A_2 & A_1 & A_0 \\ B_3 & B_2 & B_1 & B_0 \end{array}} S_2 \quad S_1 \quad S_0 \\
 \hline
 \end{array}$$

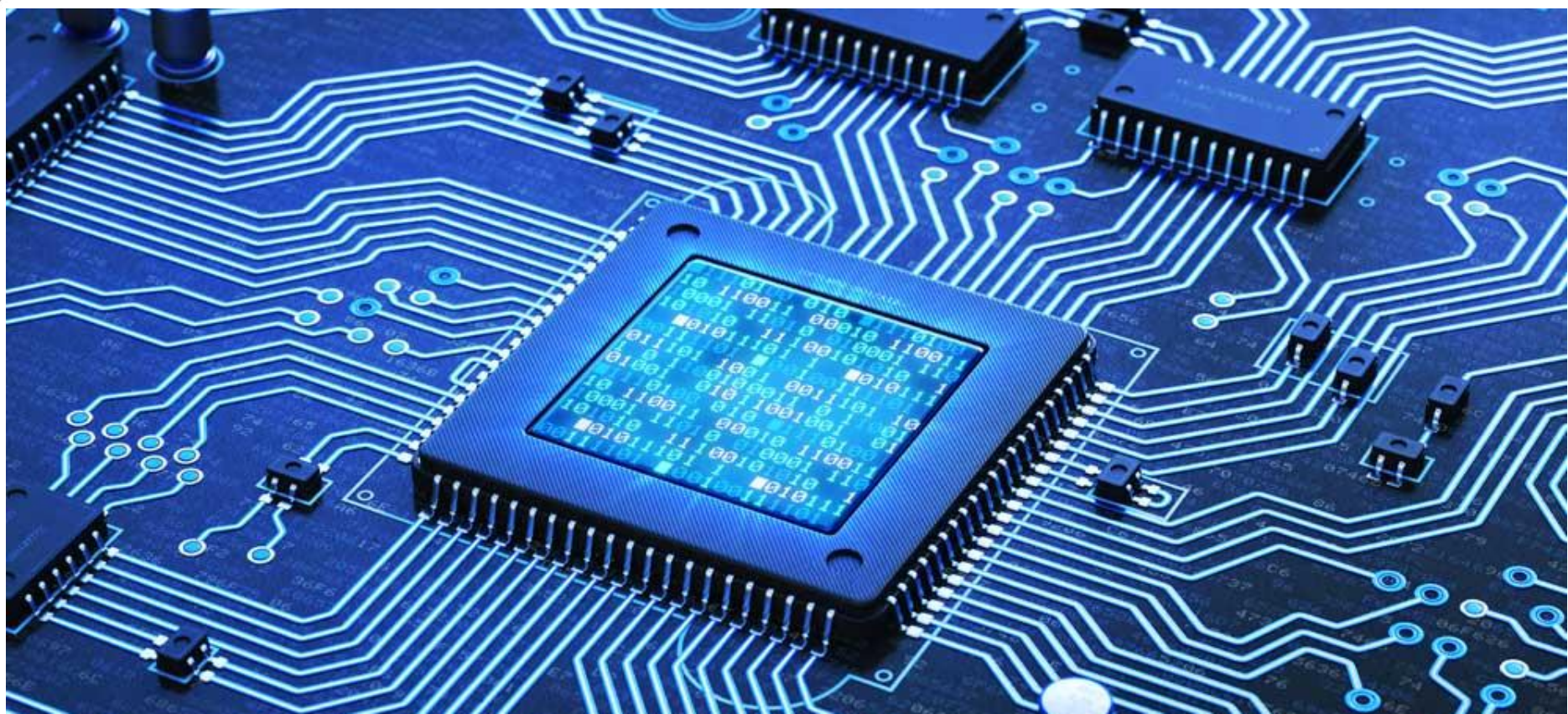
$$\begin{array}{r}
 4. \quad \begin{array}{cccc} (C_2) & (C_1) & (C_0) & \\ A_3 & A_2 & A_1 & A_0 \\ B_3 & B_2 & B_1 & B_0 \end{array} \\
 \hline
 \phantom{\begin{array}{cccc} (C_2) & (C_1) & (C_0) & \\ A_3 & A_2 & A_1 & A_0 \\ B_3 & B_2 & B_1 & B_0 \end{array}} C_3 \quad S_3 \quad S_2 \quad S_1 \quad S_0 \\
 \hline
 \end{array}$$




Binary Subtraction

Basic Rules of Binary Subtraction (Half Subtractor)

	A		B		(A-B)	
	Minuend		Subtrahend		Difference	Borrow out
Rule 1	0	—	0	=	0	
Rule 2	0	—	1	=	1	and borrow 1
Rule 3	1	—	0	=	1	
Rule 4	1	—	1	=	0	

 

Half Subtractor Logic Diagram

 

Subtraction: Borrow Bit

Inputs		Outputs	
Minuend <i>A</i>	Subtrahend <i>B</i>	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$A - B$

D_i

B_o

Binary


Decimal

borrow

Minuend
Subtrahend
Difference

10	10	2
- 0	1	- 1
0	1	1

 When 1 is subtracted from 0
A borrow is taken from the
next most significant bit, by
making it zero




Subtraction: Example

		32s	16s	8s	4s	2s	1s	
			1					
			10	10				
					0	10		
A		1	0	0	1	0	1	37
--B	-			1	0	1	0	10
D			1	1	0	1	1 ₂	27 ₁₀


Overall, the result will the Borrow bit will be cleared (zero).

Subtraction: Digital Implementation
 
$$\begin{array}{r}
 A \quad 1 \quad 0 \quad 0 \quad 1 \quad 0 \quad 1 \quad 37 \\
 -B \quad \quad \quad \quad 1 \quad 0 \quad 1 \quad 0 \quad 10 \\
 \hline
 D \quad \quad 1 \quad 1 \quad 0 \quad 1 \quad 1_2 \quad 27_{10}
 \end{array}$$



 
3-bit Binary Subtraction (Full Subtractor)




Inputs			Outputs	
Minuend (A)	Subtrahend (B)	Borrow-in (B_{in})	Difference (D)	Borrow-out (B_o)
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Subtraction: Example

	64s	32s	16s	8s	4s	2s	1s	
<i>A</i>	1	1	1	0	1	0	1	117
<i>- B</i>	- 0	0	1	1	1	0	0	- 28
<i>Di</i>	1	0	1	1	0	0	1	89

 

 
- **Borrow (in)** and **Borrow (out)** are shown above



7-Segment Display Code

7-Segment Display Code

Number displayed is 3 here

 

- 1 means the segment is ON

	a	b	c	d	e	f	g
0	1	1	1	1	1	1	0
1	0	1	1	0	0	0	0
2	1	1	0	1	1	0	1
3	1	1	1	1	0	0	1
4	0	1	1	0	0	1	1
5	1	0	1	1	0	1	1
6	0	0	1	1	1	1	1
7	1	1	1	0	0	0	0
8	1	1	1	1	1	1	1
9	1	1	1	0	0	1	1
a	1	1	1	1	1	0	1
b	0	0	1	1	1	1	1
c	0	0	0	1	1	0	1
d	0	1	1	1	1	0	1
e	1	1	0	1	1	1	1
f	1	0	0	0	1	1	1

Session 2.2: Summary

- 7-Segment Display
- Logic Gates
- AND, OR, NOT
- NAND and NOR
- XOR and Exclusive-NOR
- Logic Gates - ICs
- Binary Addition
 - Half and Full Adder Circuits
- Binary Subtraction
 - Half and Full Subtractor Circuits