



# Digital Systems and Computer Architecture

## Session 2.12

### Module 2


## Mouli Sankaran

### JK and T Flip-flops
 
## Session 2.12: Focus



- Applications using D Flip-flop
  - 4-bit Asynchronous Up counter
  - 4-bit Asynchronous Down counter
  - Serial to Parallel Data Converter






# Applications using D-Flip-flops

# Quiz 1: What does this circuit do?

 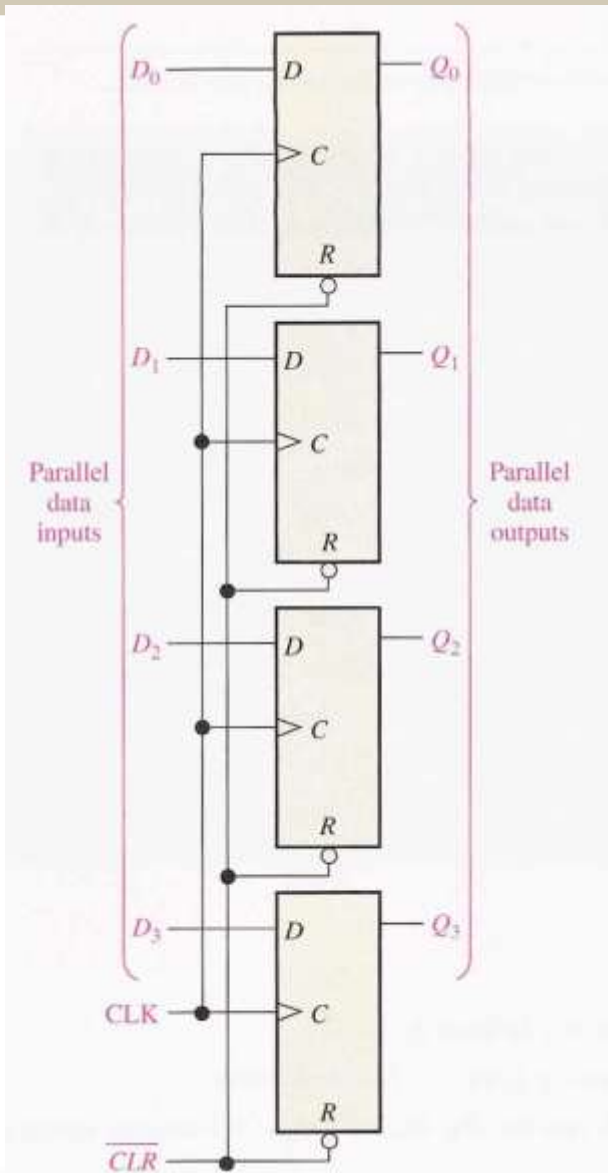

**4-bit  
Data  
storage**
 
# Example 1: 4-bit Asynchronous Up Counter




All are +ve edge triggered D flip-flops

Initially all D Flip-flops are cleared


$Q_3Q_2Q_1Q_0 = 0000$

CLK is clock input

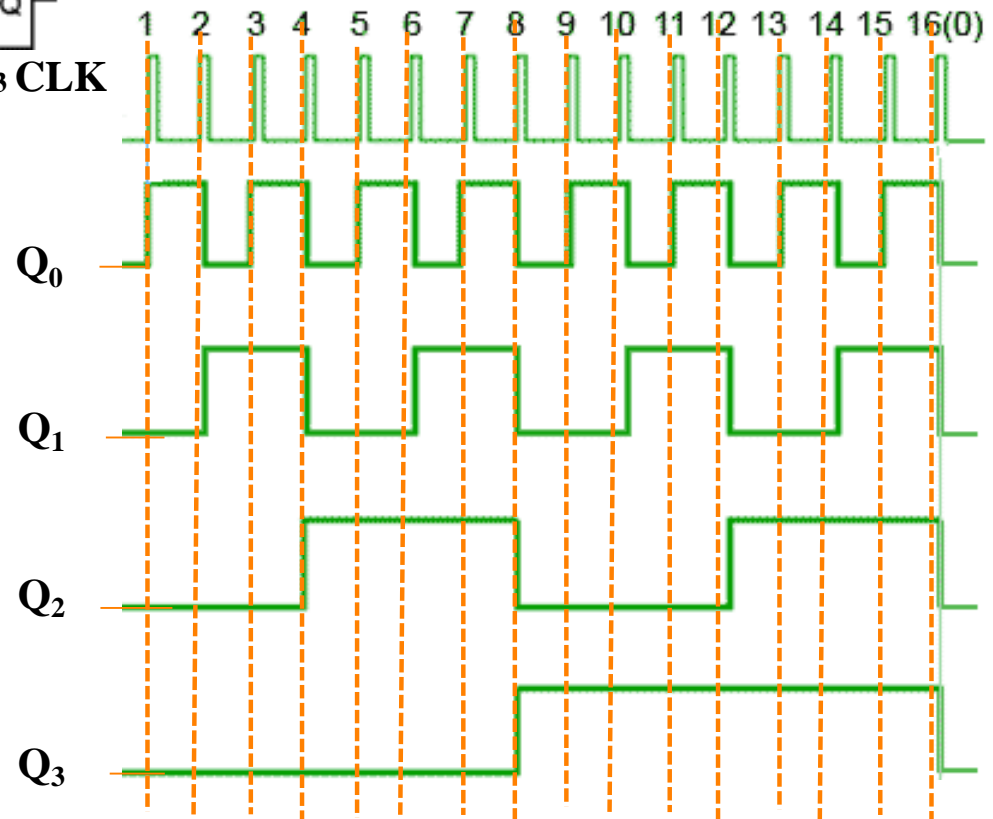- It counts the clock pulses from 0000 to 1111
- $Q'$  of previous stage is fed as clock to the next stage flip-flop
- Since the transitions of flip-flops are not happening based on the same clock pulse, this is an asynchronous counter


 
## Example 2: 4-bit Asynchronous Down Counter




- Initially all D Flip-flops are set to 1111
- It down counts the clock pulses from 1111 to 0000




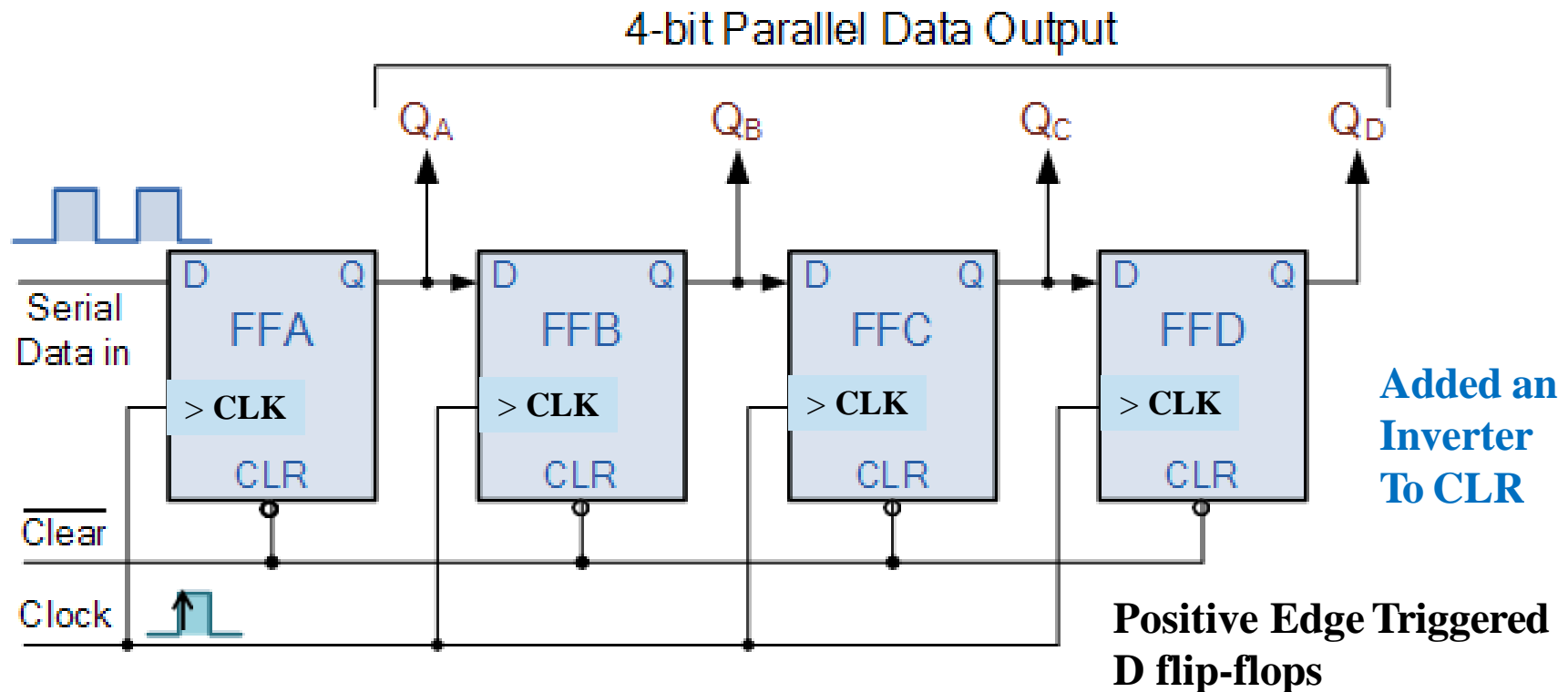
## Example 3: Serial to Parallel Data Converter



- Serial to parallel data converter
- The serial data is shifted in at the positive edge of every clock pulse
- After four clock pulses the parallel data is available at  $Q_3Q_2Q_1Q_0$

## Session 2.12: Summary

- Applications using D Flip-flop
  - 4-bit Asynchronous Up counter
  - 4-bit Asynchronous Down counter
  - Serial to Parallel Data Converter