



# Digital Systems and Computer Architecture

## Session 2.5

### Module 2


## Mouli Sankaran

### SOP and POS forms of Boolean Expressions
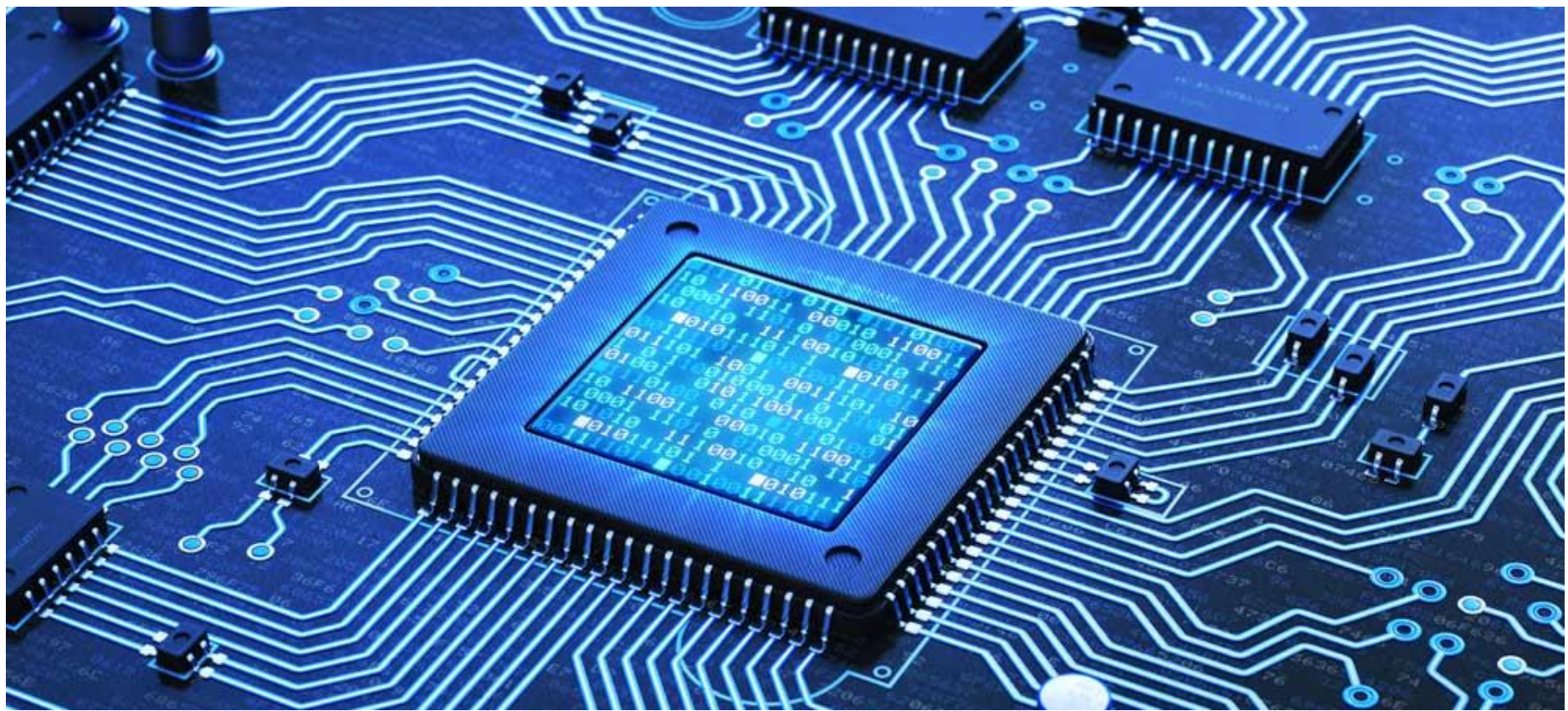
## Session 2.5: Focus

- Simplification Techniques
- Simplification using Boolean Algebra
  - Quiz 1 to 3
- Two forms of Boolean Expressions
  - Sum-of-Products (minterms)
  - Products-of-Sums (maxterms)
  - Canonical notation
  - Example
- Home Work






# Introduction to Boolean Algebra

## Recap: Variables, Literals and Terms

- **Variables** are different symbols in a **Boolean expression**
  - They may take on the values **'0'** or **'1'**
  - **Complement** of a variable is **not** considered as a **separate variable**
  - Each occurrence of a **variable** or its **complement** is called a **literal**
  - A **term** is the **expression formed by literals and operations at one level.**
  - Each **term** requires a **gate** and each **variable within the term** designates an **input to the gate**
- $$\overline{A} + A.B$$

<b>Variables</b>	<b>: 2</b>
<b>Literals</b>	<b>: 3</b>
<b>Terms</b>	<b>: 2</b>



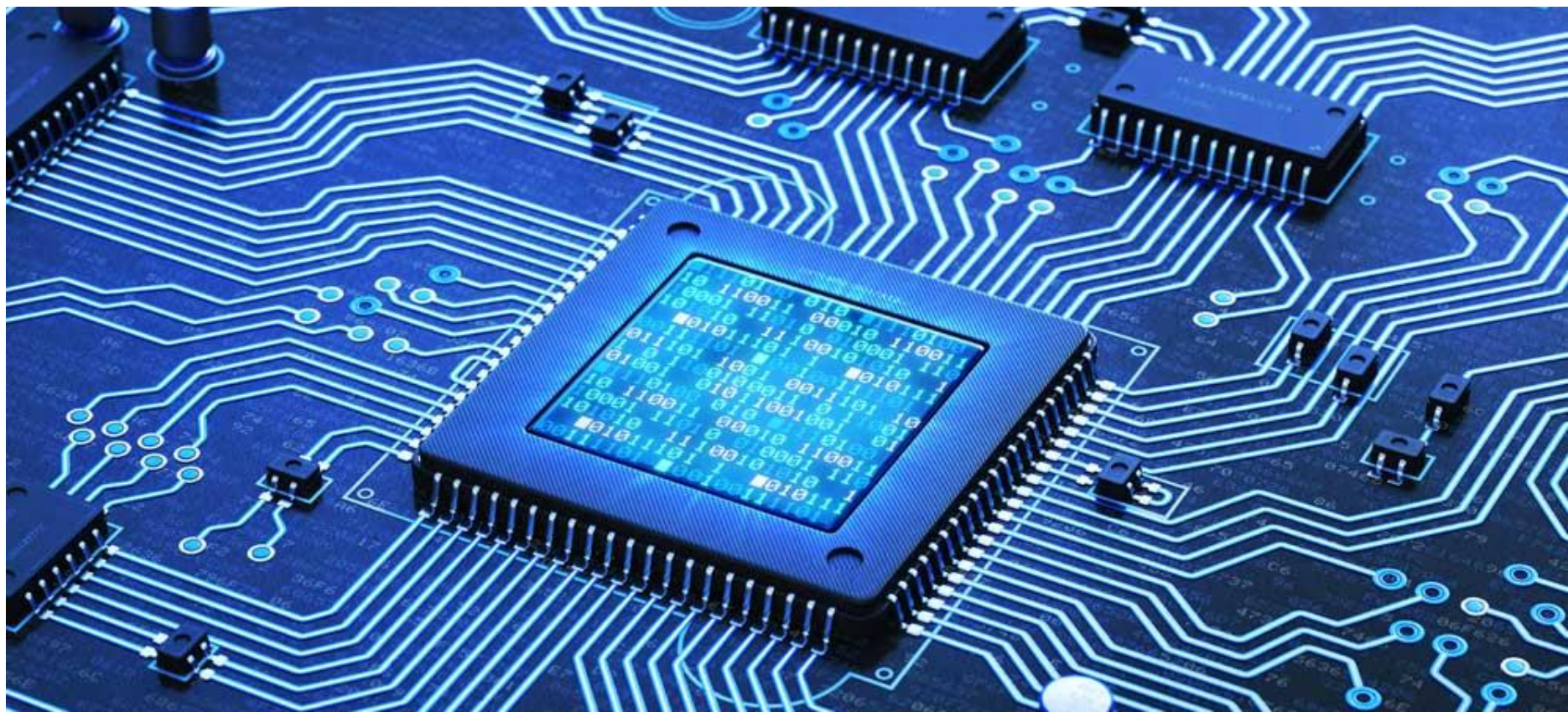

# Simplification Techniques


# Need for Simplification

- Simplification means simplifying or more precisely minimizing a given complex Boolean expression
- The **primary objective** of all simplification procedures is to **obtain** an expression that has the **minimum number of terms**
  - A simplified Boolean expression uses the fewest gates possible to implement a given expression
  - If gates are reduced, the complexity of the implementation as well as power consumption are also reduced
- Obtaining an expression with the **minimum** number of **literals** or **symbols** is usually the **secondary objective**
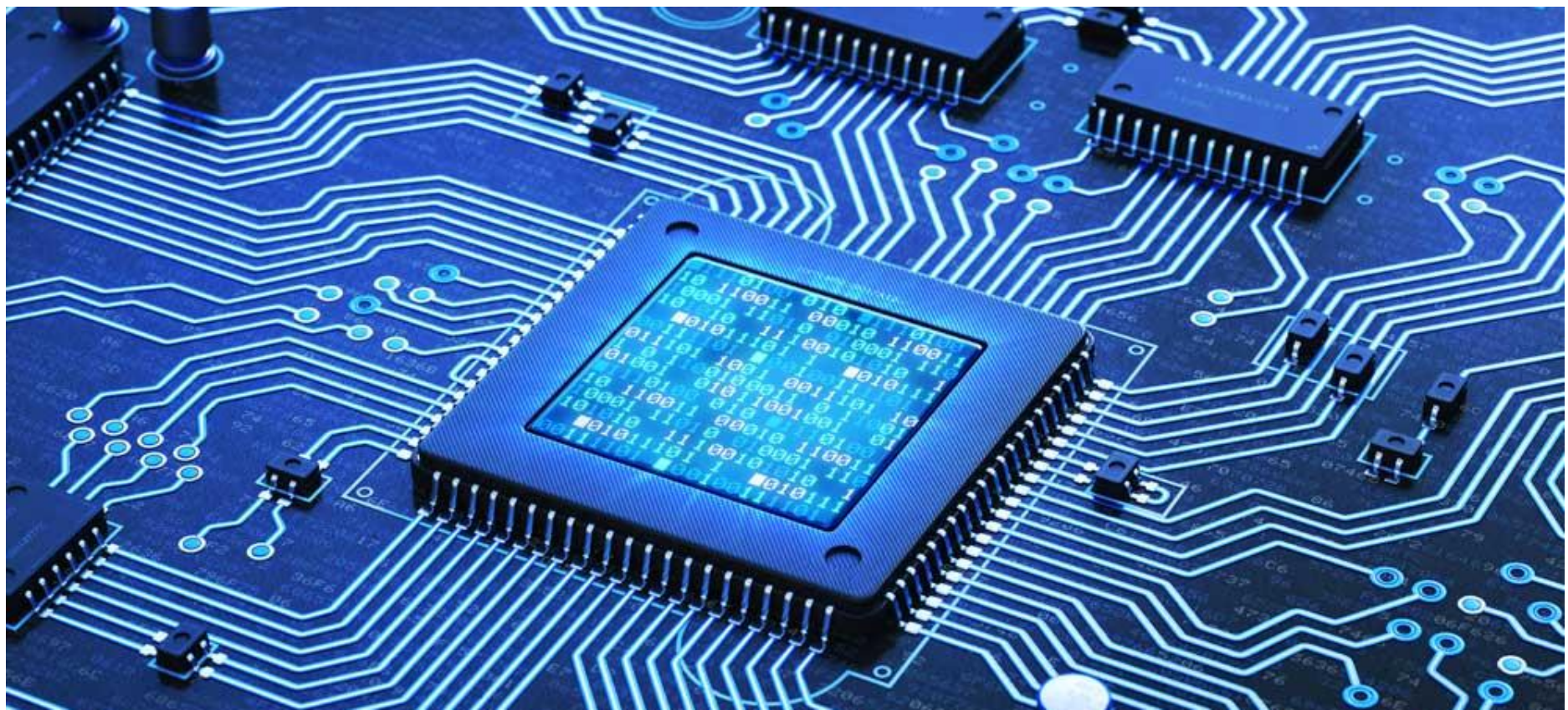
# Simplification Techniques

- Simplification using Boolean algebra
- Other two popular methods are:
  - The Quine–McCluskey tabular method;
  - The Karnaugh map method





# Simplification Using Boolean Algebra



# Simplification Using Boolean Algebra

- The approach taken in this section is to
  - Use the basic laws, rules and theorems of Boolean Algebra
  - To manipulate and simplify an Expression
  - Which will result in less number of gates/literals without changing the function of the original Boolean Expression
- A **simplified** Boolean Expression **uses the fewest gates possible to implement** a given expression

# Quiz 1: Simplify the Boolean Expression

- Simplify the expression:  $AB + A(B+C) + B(B+C)$
- **Step 1:** Apply Distributive law to 2<sup>nd</sup> and 3<sup>rd</sup> items
  - $AB + \mathbf{AB} + \mathbf{AC} + \mathbf{BB} + \mathbf{BC}$
- **Step 2:** Apply **rule 7** ( $BB = B$ )
  - $AB + AB + AC + \mathbf{B} + BC$
- **Step 3:** Apply **rule 5** ( $AB + AB = AB$ )
  - $\mathbf{AB} + AC + B + BC$
- **Step 4:** Apply **rule 10** ( $B + BC = B$ )
  - $AB + AC + \mathbf{B}$
- **Step 5:** Apply **rule 10** ( $AB + B = B$ )
  - $\mathbf{AC + B}$

**Note:** The terms in **Bold** are the ones affected by the rules in each step.



## Quiz 2: Simplify the Boolean Expression

- Simplify the expression:  $[\overline{A}\overline{B}(C + BD) + \overline{A}\overline{B}]C$
- **Step 1:** Apply Distributive law to the terms within brackets
  - $(\overline{A}\overline{B}C + \overline{A}\overline{B}BD + \overline{A}\overline{B})C$
- **Step 2:** Apply **rule 8** ( $B\overline{B} = 0$ )
  - $(\overline{A}\overline{B}C + A \cdot 0 \cdot D + \overline{A}\overline{B})C$
- **Step 3:** Apply **rule 3** ( $A \cdot 0 \cdot D = 0$ )
  - $(\overline{A}\overline{B}C + 0 + \overline{A}\overline{B})C$
- **Step 4:** Apply **rule 1** (drop the 0)
  - $(\overline{A}\overline{B}C + \overline{A}\overline{B})C$
- **Step 5:** Apply Distributive law
  - $\overline{A}\overline{B}CC + \overline{A}\overline{B}C$

## Quiz 2 ... contd

- Simplify the expression:  $[A\bar{B}(C + BD) + \bar{A}\bar{B}]C$
- **From Step 5:**  $A\bar{B}CC + \bar{A}\bar{B}C$
- **Step 6:** Apply **rule 7** ( $CC = C$ ) to the first term
  - $A\bar{B}C + \bar{A}\bar{B}C$
- **Step 7:** Factor out  $\bar{B} C$ 
  - $\bar{B}C(A + \bar{A})$
- **Step 8:** Apply **rule 6** ( $A + \bar{A} = 1$ )
  - $\bar{B}C \cdot 1$
- **Step 9:** Apply **rule 4** (drop the 1)
  - $\bar{B}C$




## Quiz 3: Simplify the Boolean Expression

- Simplify the expression:  $\overline{AB + AC + \bar{A}\bar{B}C}$
- **Step 1:** Apply DeMorgan's theorem to the first term
  - $(\overline{AB})(\overline{AC}) + \bar{A}\bar{B}C$
- **Step 2:** Apply DeMorgan's theorem to each term in parenthesis
  - $(\bar{A} + \bar{B})(\bar{A} + \bar{C}) + \bar{A}\bar{B}C$
- **Step 3:** Apply Distributive law to the terms within parenthesis
  - $\bar{A}\bar{A} + \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{B}C$
- **Step 4:** Apply **rule 7** ( $\bar{A}\bar{A} = \bar{A}$ ) to the first term
  - $\bar{A} + \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{B}C$
- **Step 5:** Apply **rule 10** ( $A + AB = A$ ) to the 3<sup>rd</sup> and last terms
  - $\bar{A} + \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{B}\bar{C}$
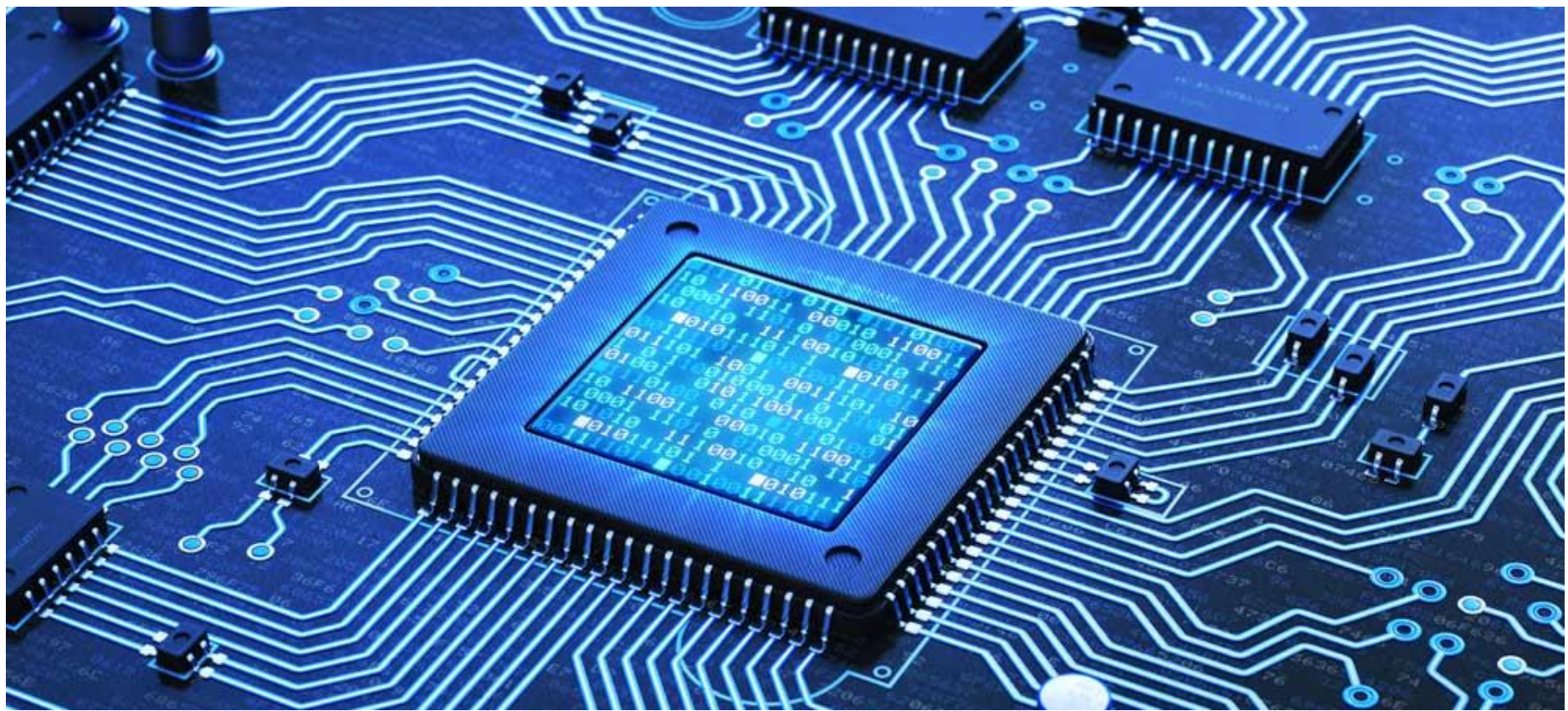
## Quiz 3 ... contd.

- From **Step 5**:  $\bar{A} + \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{B}\bar{C}$
- **Step 6**: Apply **rule 10** ( $A + AB = A$ ) to the 1<sup>st</sup> and 2<sup>nd</sup> terms
  - $\bar{A} + \bar{A}\bar{B} + \bar{B}\bar{C}$
- **Step 7**: Apply **rule 10** ( $A + AB = A$ ) to the 1<sup>st</sup> and 2<sup>nd</sup> terms
  - $\bar{A} + \bar{B}\bar{C}$





# Two Forms of Boolean Expressions

# Two Forms of Boolean Expressions

- Boolean Expressions are normally expressed in one of these forms for Simplification
  - **Sum-of-Products (SOP)**
  - **Product-of-Sums (POS)**
- Let us see them before studying other Simplification techniques



# Sum-of-Products

- **Sum-of-products** expression contains the **sum** of different **terms**, with each term being either a **single literal** or a **product of more than one literal**
- It can be obtained from the **truth table** directly by considering those **input combinations** that produce a **logic '1'** at the **output**.
- Each such input combination produces a term, which are called **minterms**
- A **minterm** is a combination of variables that produces a **1** in the function and then taking the **OR** of **all those terms**

## Example: Sum-of-Products


- For Example **Truth table** below can be expressed as:
  - Only those terms which produce an **output** of **1**

<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$$Y = \overline{A} . \overline{B} . \overline{C} + \overline{A} . B . C + A . B . \overline{C} + A . \overline{B} . C$$

# Implementation of Sum-of-Products

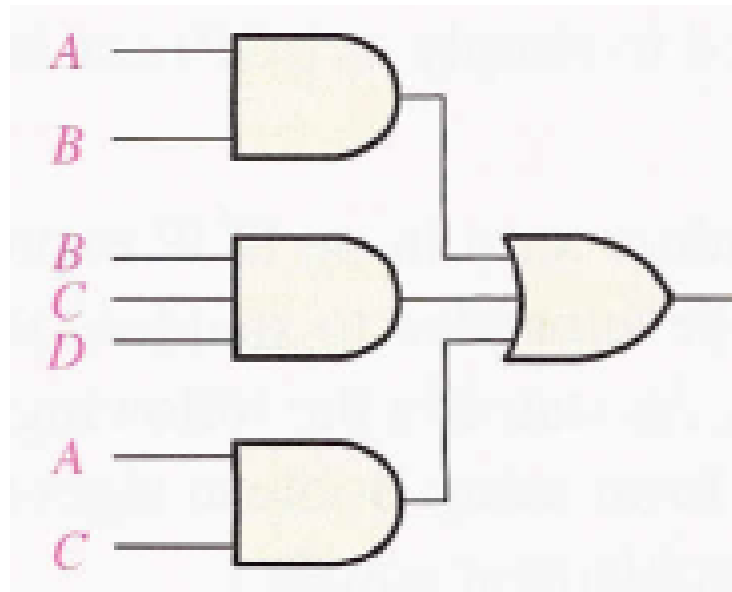- **Example:**  $AB + BCD + AC$  can be implemented as shown below:



**AND-OR**



## Quiz 4: Is this in SOP or POS form?

- $\overline{ABC} + A\overline{BC}$ : **Neither in SOP nor POS form!!**

For an expression to properly follow the **SOP** or **POS** canonical form, **no complementation bar** should **cover more than one variable!**

# Minterms of Three Binary Variables

- All the combinations of Sum-of-Products of three variables and their nomenclature are given below

<i>x</i>	<i>y</i>	<i>z</i>	Minterms	
			Term	Designation
0	0	0	$x'y'z'$	$m_0$
0	0	1	$x'y'z$	$m_1$
0	1	0	$x'yz'$	$m_2$
0	1	1	$x'yz$	$m_3$
1	0	0	$xy'z'$	$m_4$
1	0	1	$xy'z$	$m_5$
1	1	0	$xyz'$	$m_6$
1	1	1	$xyz$	$m_7$

# Product-of-Sums

- **Product-of-Sums** expression contains the **product** of different **terms**, with each term being either a **single literal** or a **sum of more than one literal**
- It can be obtained from the **truth table** directly by considering those **input combinations** that produce a **logic '0'** at the **output**.
- Each such input combination produces a term, which are called **maxterms**
- A **maxterm** is a combination of variables that produces a **0** in the function and then taking the **AND** of **all those terms**
- Boolean functions expressed as a **sum of minterms** or **product of maxterms** are said to be in **canonical form**

## Example: Product-of-Sums

- For Example **Truth table** below can be expressed as:

<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0


$$Y = (A + B + \overline{C}).(A + \overline{B} + C).(\overline{A} + B + C).(\overline{A} + \overline{B} + \overline{C})$$



# Implementation of Product-of-Sums

- **Example:**  $(A + B) \cdot (B + C + D) \cdot (A + C)$

**OR-AND**

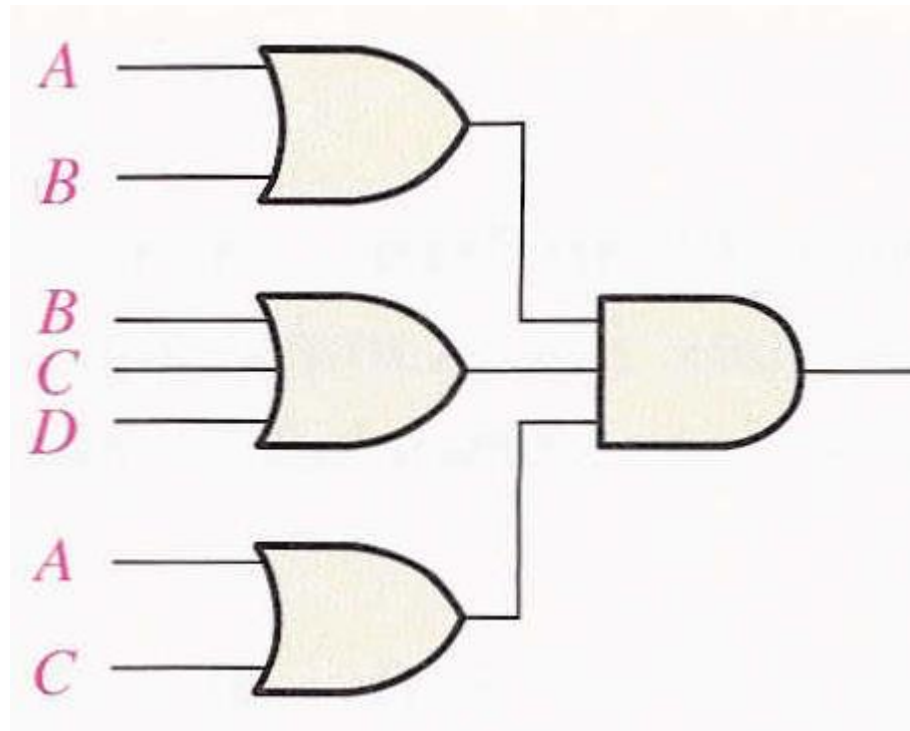


# Maxterms of Three Binary Variables

- All the combinations of Product-of-Sums of three variables and their nomenclature are given below



Minterms							Maxterms	
Term	Designation	$x$	$y$	$z$	Term	Designation		
$x'y'z'$	$m_0$	0	0	0	$x + y + z$	$M_0$		
$x'y'z$	$m_1$	0	0	1	$x + y + z'$	$M_1$		
$x'yz'$	$m_2$	0	1	0	$x + y' + z$	$M_2$		
$x'yz$	$m_3$	0	1	1	$x + y' + z'$	$M_3$		
$xy'z'$	$m_4$	1	0	0	$x' + y + z$	$M_4$		
$xy'z$	$m_5$	1	0	1	$x' + y + z'$	$M_5$		
$xyz'$	$m_6$	1	1	0	$x' + y' + z$	$M_6$		
$xyz$	$m_7$	1	1	1	$x' + y' + z'$	$M_7$		

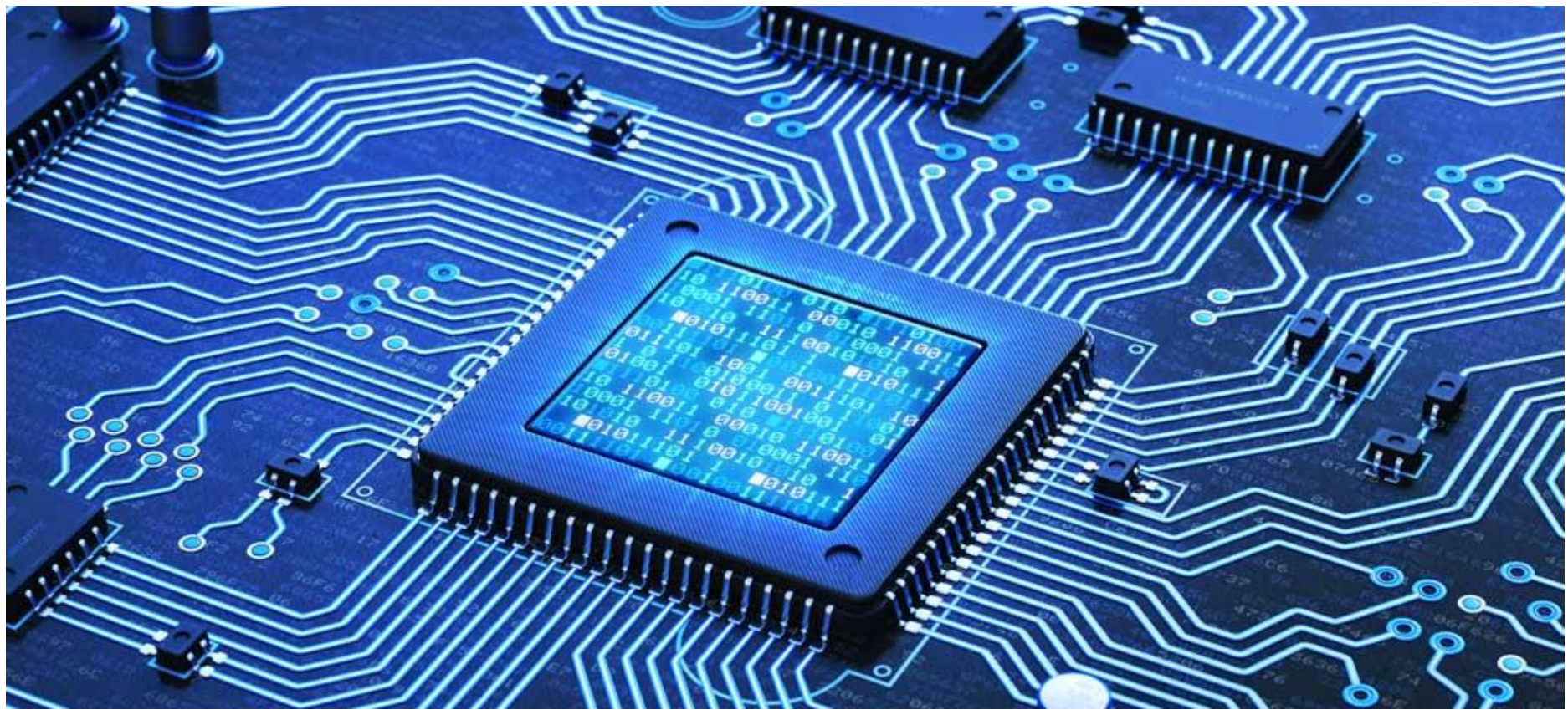

# Examples

## Another Example

$$f_1 = x'y'z + xy'z' + xyz = m_1 + m_4 + m_7$$


$$f_2 = x'yz + xy'z + xyz' + xyz = m_3 + m_5 + m_6 + m_7$$

<b>x</b>	<b>y</b>	<b>z</b>	<b>Function <math>f_1</math></b>	<b>Function <math>f_2</math></b>
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{aligned} f_1 &= (x + y + z)(x + y' + z)(x' + y + z')(x' + y' + z) \\ &= M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6 \end{aligned}$$
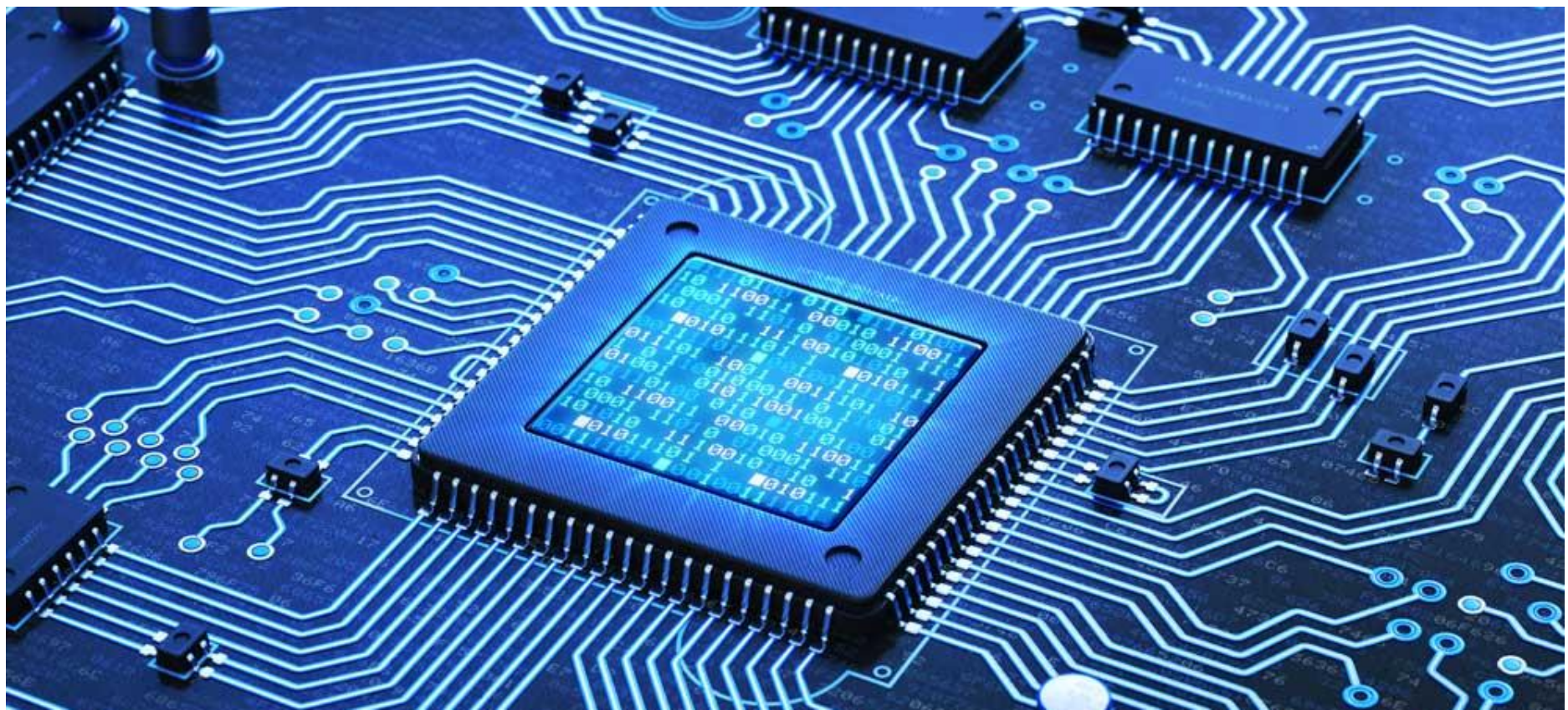
$$\begin{aligned} f_2 &= (x + y + z)(x + y + z')(x + y' + z)(x' + y + z) \\ &= M_0 M_1 M_2 M_4 \end{aligned}$$





# Home Work

# Home Work

- **Simplify** the following Boolean Expressions, using Boolean Algebra:
- 1.  $\bar{A}BC + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}C + ABC$ 
  - Solution:  $AC + BC + \bar{B}\bar{C}$  or  $BC + A\bar{B} + \bar{B}\bar{C}$
- 2.  $xy + x'z + yz$ 
  - Solution:  $xy + x'z$ .
- 3.  $(x + y)(x + y')$ 
  - Solution:  $x$

**Note:** For the problem 1, both the above solutions are correct.

You can verify this by constructing a truth table.

The reason for getting different simplified equations is the order we apply the rules and the terms that we take up first.

## Session 2.5: Summary

- Simplification Techniques
- Simplification using Boolean Algebra
  - Quiz 1 to 3
- Two forms of Boolean Expressions
  - Sum-of-Products (minterms)
  - Products-of-Sums (maxterms)
  - Canonical notation
  - Example
- Home Work