



# Digital Systems and Computer Architecture


## Session 1.3

**Module 1a:** Kirchhoff's Laws, Resistors in Series and Parallel
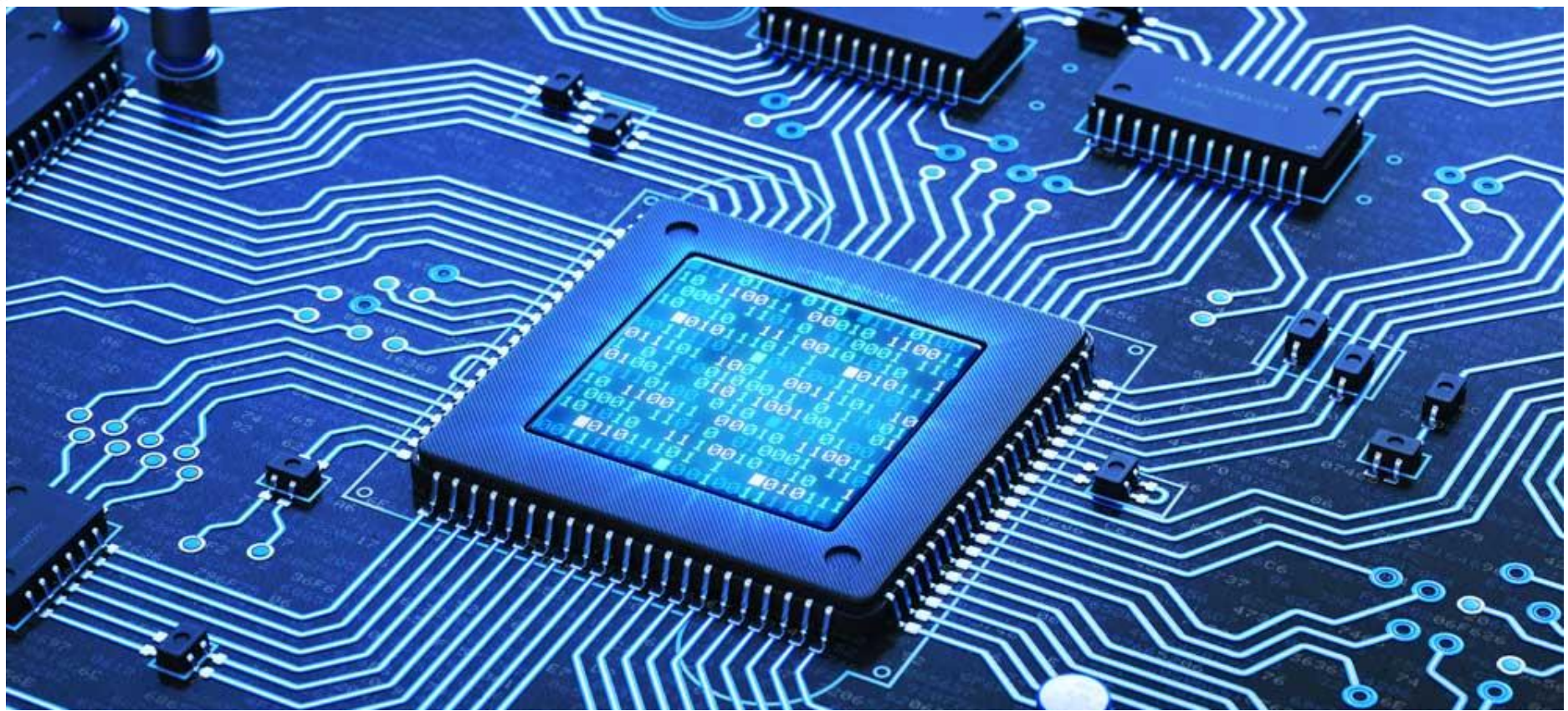
## Session 1.3: Focus

- Conservation of Energy
- Kirchhoff's Current Law
- Kirchhoff's Current Law
- Resistors in Series and Parallel






# Conservation of Energy
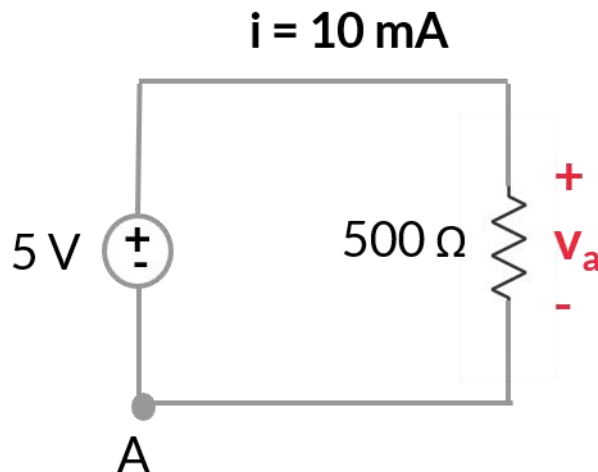
# Conservation of Energy

- The law of conservation of energy states that the total energy of an isolated system remains constant; it is said to be conserved over time.
  - Total power supplied + Total power absorbed = 0
  - $P_S + P_A = 0$




$$P_A = (i^2 * R) = ((10 * 10^{-3})^2 * 500) = 50 \text{ mW}$$

$$P_S = -(v * i) = -(5 * 10 * 10^{-3}) = -50 \text{ mW}$$
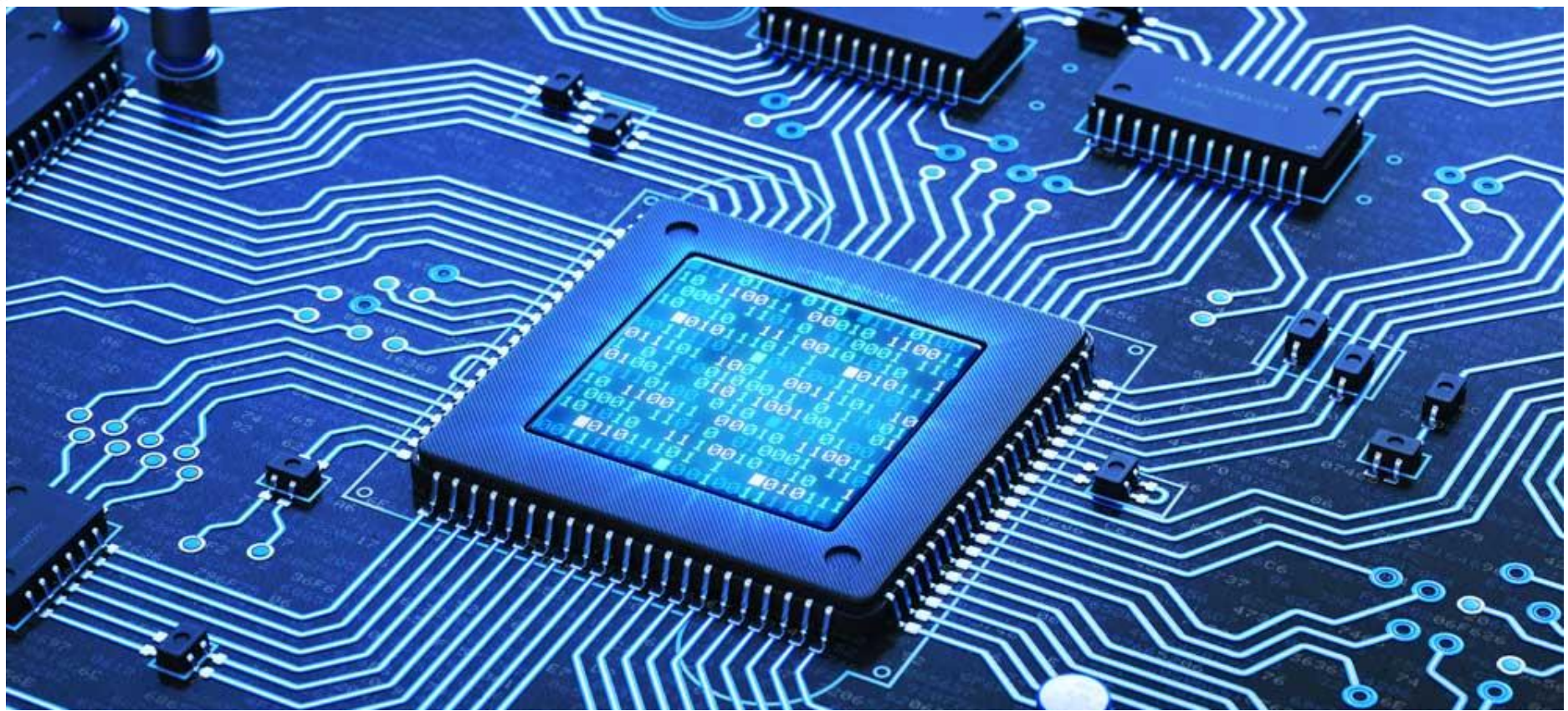
$$P_S + P_A = -50 \text{ mW} + 50 \text{ mW} = 0$$





## Kirchhoff's Voltage Law (KVL)

# Kirchhoff's Voltage Law

- **The algebraic sum of the voltages around any closed path is zero.**
- If we trace out a closed path, the algebraic sum of the voltages across the individual elements around it must be zero.


$$V_1 + V_2 + V_3 + \dots + V_n = 0$$

$$\sum_{n=1}^N v_n = 0$$

- **Algebraic sum** means that the polarity of the voltages seen while traversing the path is taken care of while adding them up.
- For **example**, the algebraic sum of the voltages of the given circuit, starting from B, in the clockwise direction, is written as:


- $-V_a + V_b - V_c = 0$

- **Thus,  $V_a = V_b - V_c$**

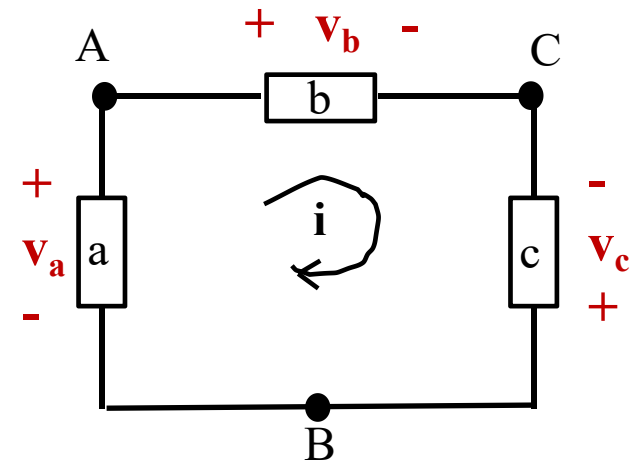
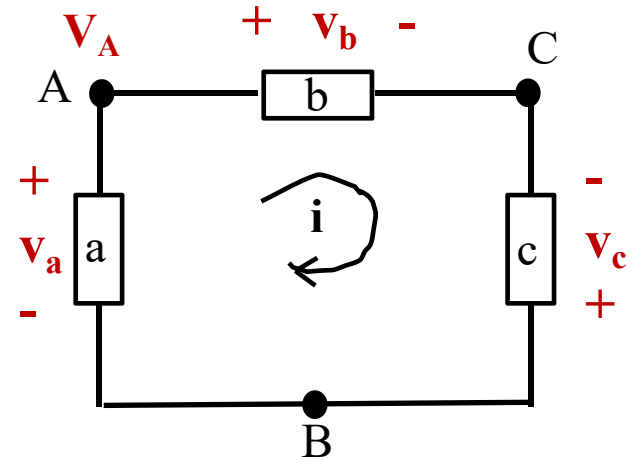
# Proof: KVL


- There is a single **unique value** for any **voltage** in a **circuit**.
- Thus, the **energy** required to **move** an **unit charge** from any point **B** to any other point **A** in a circuit, must have a value **independent** of the **path chosen** to move from **B** to **A**.



- Potential at A with respect to B through element a =  $V_A = -v_a$
- Potential at A with respect to B through elements c and b =  $V_A$
- $= v_c - v_b$
- If we equate them, we get:  $-v_a = v_c - v_b \rightarrow v_a = v_b - v_c$ 
  - Thus, we get the same value that we got when we did algebraic sum of voltages around the closed path.
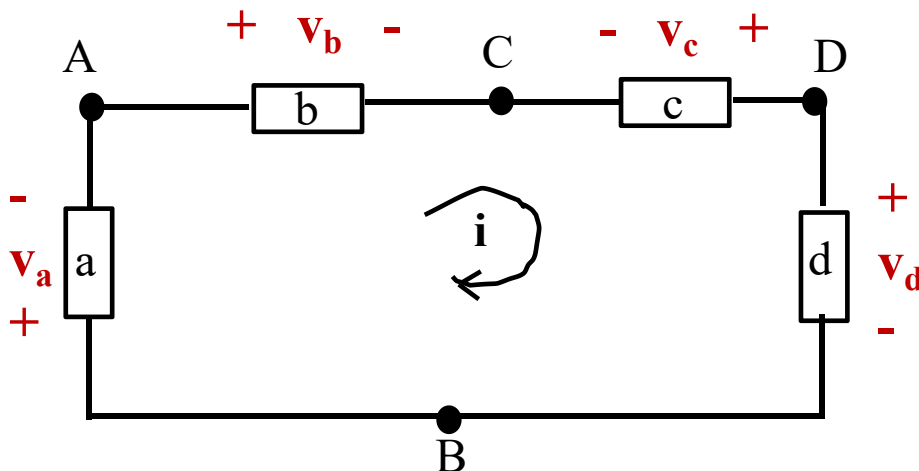
## Example 1: Applying KVL to a Circuit

- One **method** that leads to **least error** while writing the **KVL** equation is the following:
- **Moving** mentally around the **closed path** in a **clockwise direction** and writing down directly the **voltages** of each element whose **(+)** **terminal** is entered, and
- Writing down the **negative** of every **voltage** first met at the **(-)** **terminal** is entered.



Start from B and move  
in the clockwise direction

$$V_a + V_b - V_c + V_d = 0$$


It can be written as:

$$V_c = V_a + V_b + V_d$$


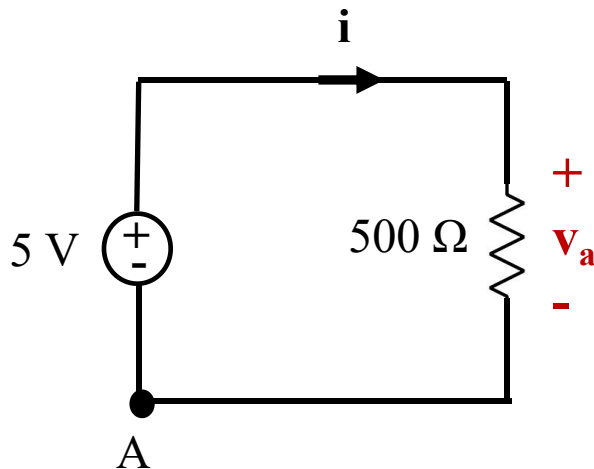
# Problem 1: KVL

- Find  $i$  and Power Supplied ( $P_s$ ) by voltage source:



Start from the node A and move in the clockwise direction till reaching A again.

$$- 5 + (i * 500) = 0 \quad : \text{KVL and Ohm's law}$$

$$i = 5 / 500 = \mathbf{10 \text{ mA}}$$

**Note:** By convention power supplied is a negative quantity.


$$P_s = - (v * i) = - (5 * 10 * 10^{-3}) = \mathbf{- 50 \text{ mW}}$$

**Ans: 10 mA and - 50 mW**
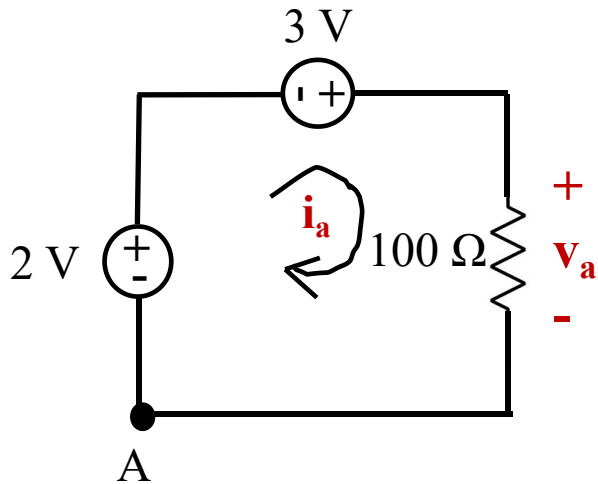
## Problem 2: KVL

- Find  $v_a$  and  $i_a$  :

Start from the node A and move in the clockwise direction till reaching A again.




$$- 2 - 3 + v_a = 0 \quad \text{:Applying KVL}$$

$$v_a = 5 \text{ V}$$

$$i_a = v_a / 100 = 5 / 100$$

$$i_a = 50 \text{ mA}$$

**Ans: 5 V and 50 mA**

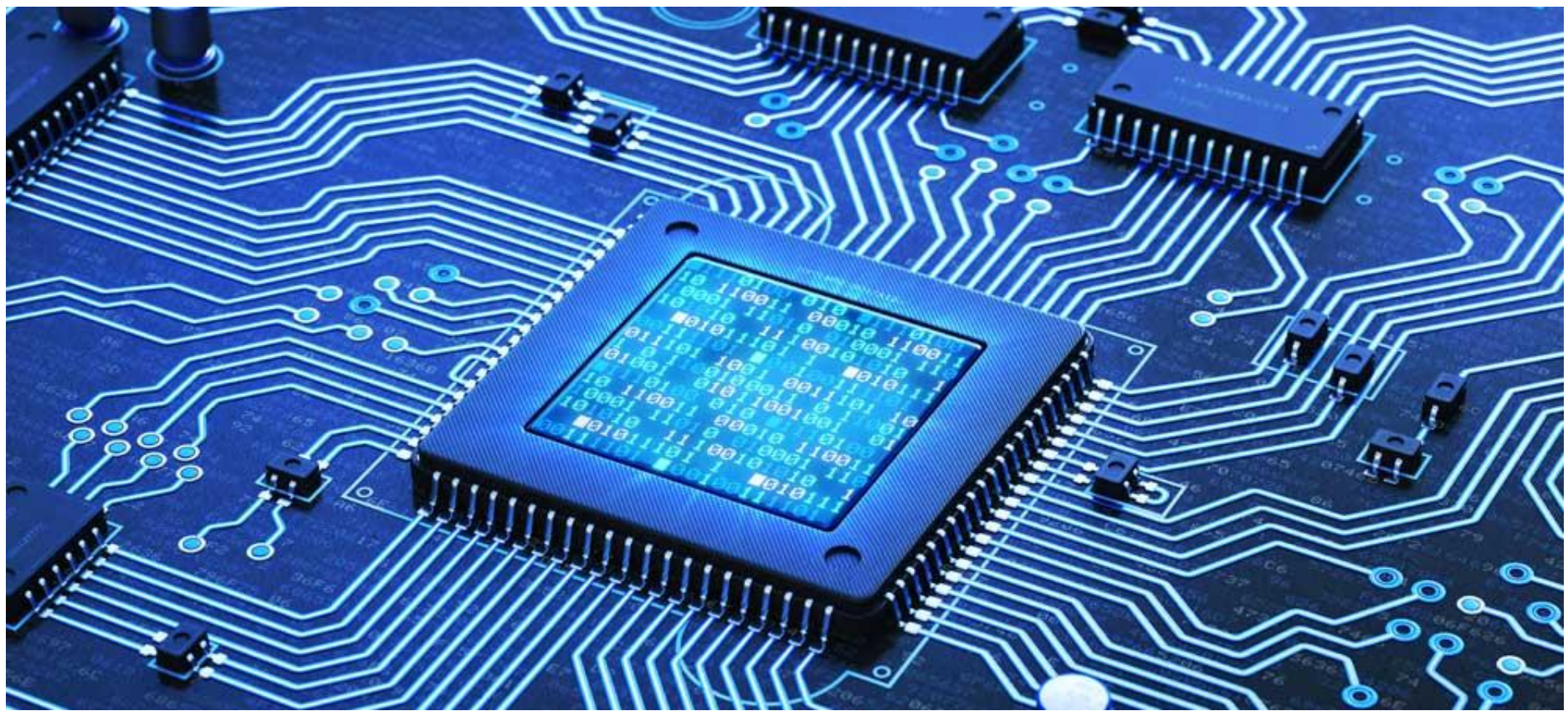


## Kirchhoff's Current Law (KCL)


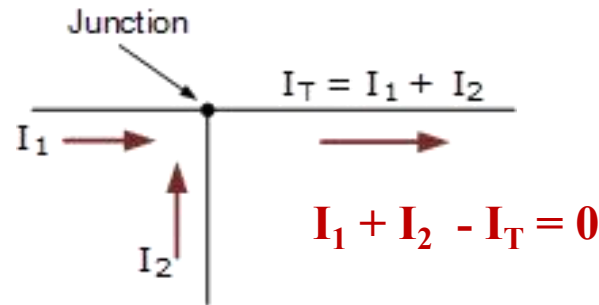
# Kirchhoff's Current Law (KCL)

- **KCL states that the algebraic sum of the currents entering any node is zero.**




$$i_1 + i_2 + i_3 + \dots + i_n = 0$$

$$\sum_{n=1}^N i_n = 0$$

- This mathematical statement proves the fact that **charges cannot accumulate at a node.**
- A **node is not a circuit element**, and it certainly **cannot store, destroy, or generate charge.**
- Hence, the currents must sum to zero at any node in the circuit

# KCL: Algebraic Sums

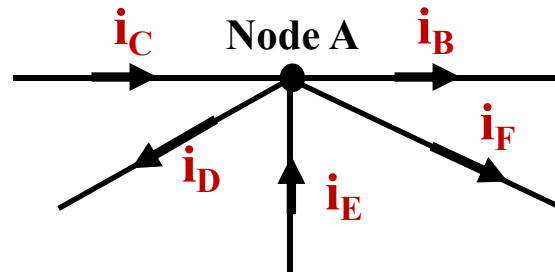


- The **algebraic sum** of the four **currents entering the node** must be **zero**:

$$i_C + i_E + (-i_D) + (-i_F) + (-i_B) = 0$$

- Similarly, this law could equally be well applied to the **algebraic sum of the currents leaving the node**:

$$i_D + i_F + i_B + (-i_C) + (-i_E) = 0$$

# Example: KCL

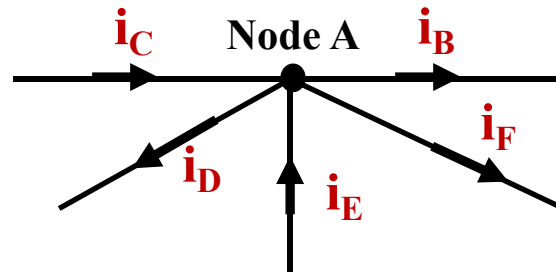


**Current entering the node A = Current leaving the node A**

$$i_C + i_E = i_B + i_D + i_F$$



## Problem 3: KCL

- Find the current  $i$ :

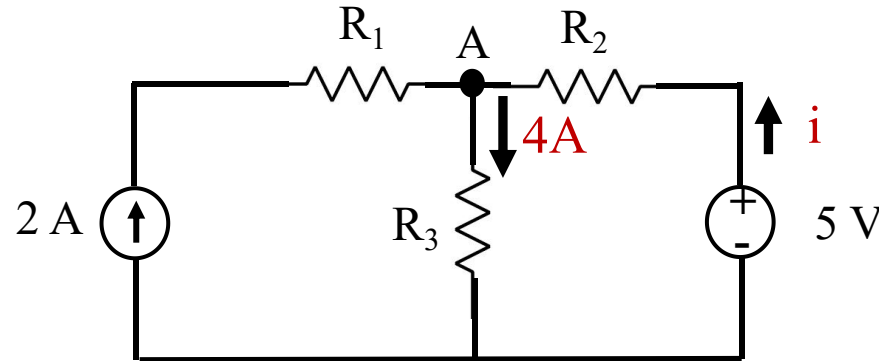


- The total current entering the node  $A = 2 + i$
- The total current leaving the node  $A = 4 \text{ A}$
- As per KCL, total current entering a node is equal to the total current leaving the node.
- Thus,  $2 + i = 4$ , then  $i = 2 \text{ A}$

Give  $V_A$  in terms of circuit elements


**ANS:  $i = 2 \text{ A}$**

$$V_A = 4 * R_3 \quad V_A = -i R_2 + 5$$

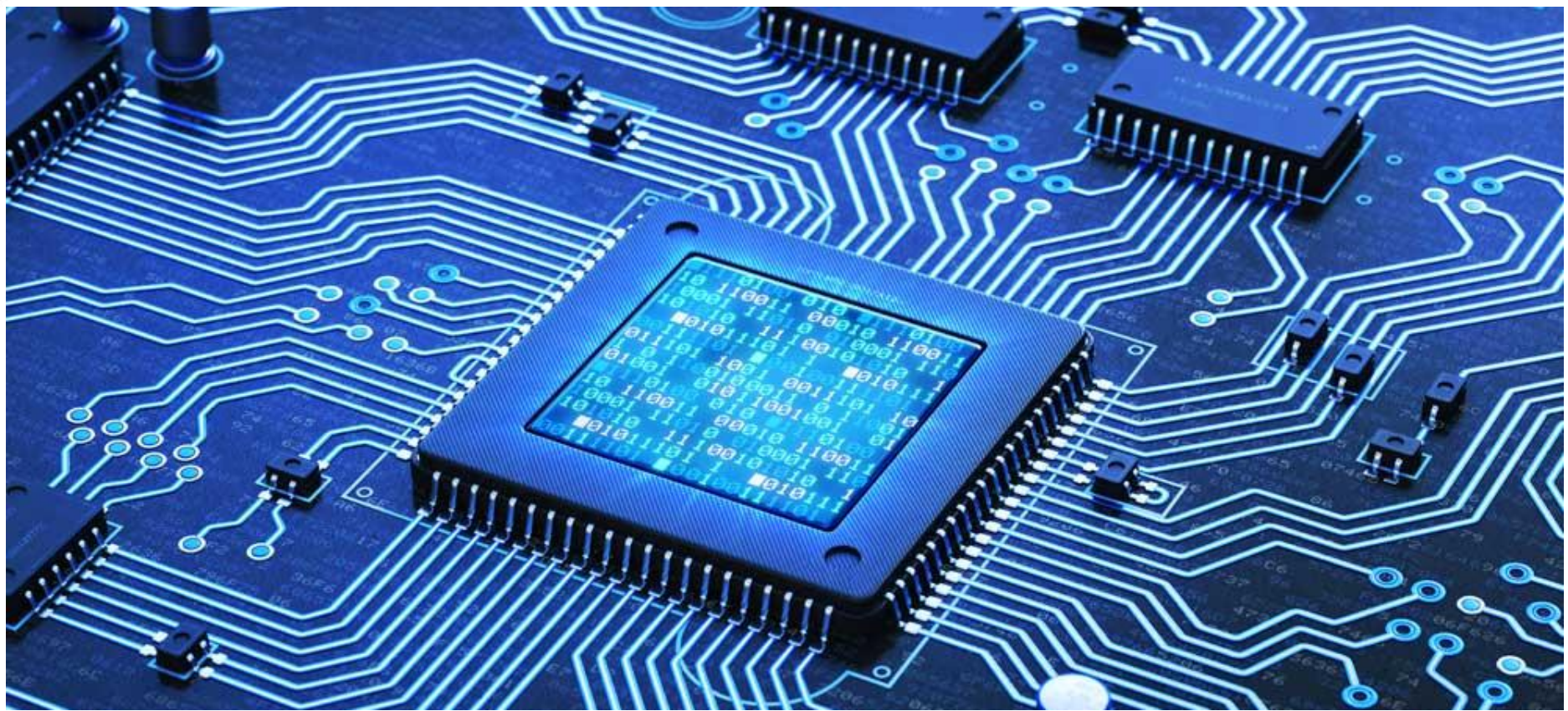

# Resistors in Series


# Combining of Resistors

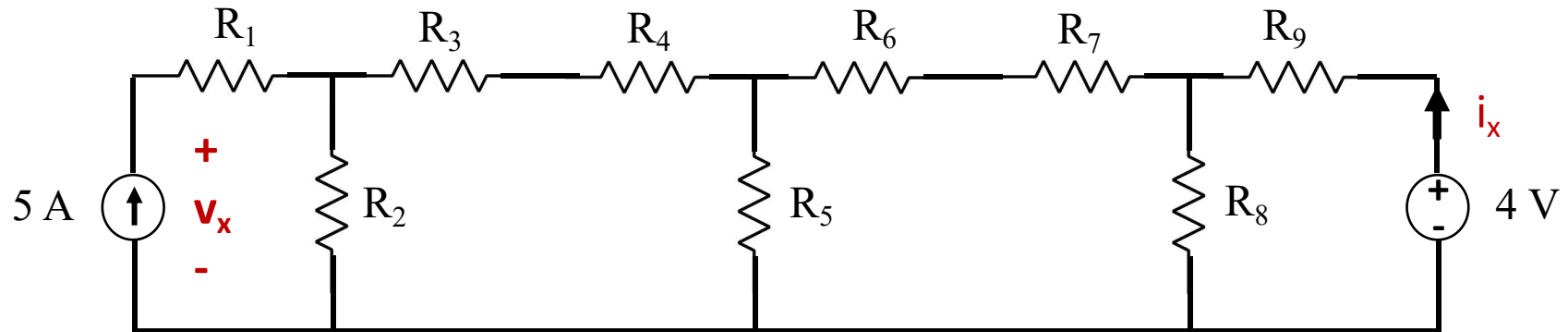

- It is often possible to **replace** relatively complicated **resistor combinations** with a single equivalent resistor.
- This is useful when we are not specifically interested in the current, voltage, or power associated with any of the individual resistors in the combinations.
- All the current, voltage, and power relationships in the remainder of the circuit will be unchanged.




# Derivation: Resistors in Series

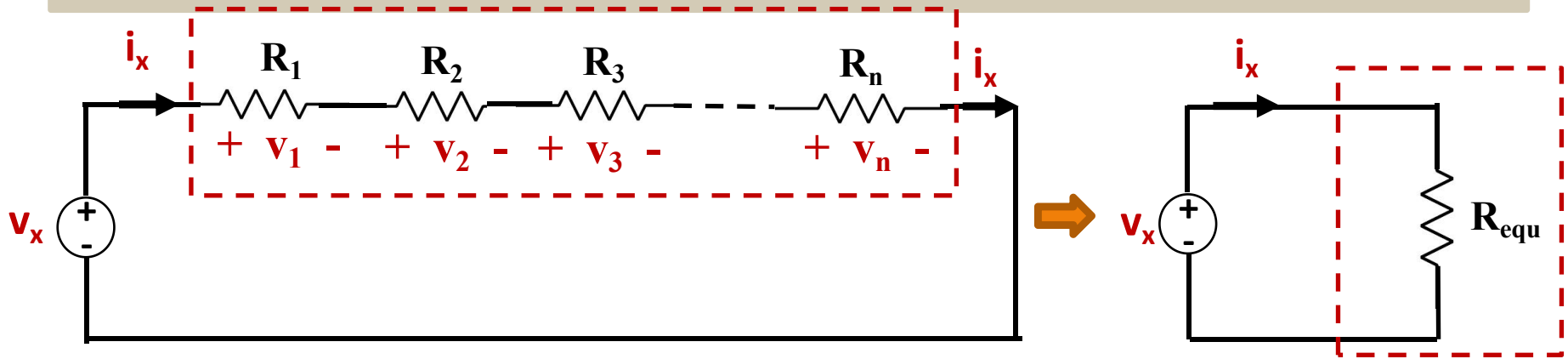

- The current  $i_x$  flowing through all the resistors in series is the **same**.
- Applying **KVL** we get:
  - $v_x = v_1 + v_2 + v_3 \dots + v_n$
- Using Ohm's law:
  - $v_x = i_x R_1 + i_x R_2 + i_x R_3 \dots + i_x R_n = i_x (R_1 + R_2 + R_3 \dots + R_n)$
  - $v_x = i_x R_{equ}$
- $R_{equ} = R_1 + R_2 + R_3 \dots + R_n$

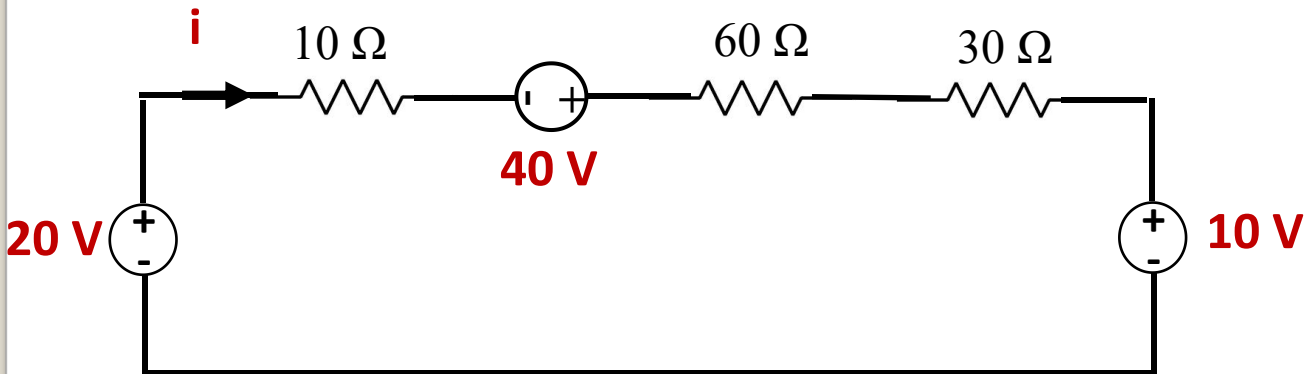
## Problem 4: Resistors in Series


- Use **source** and **resistor combinations** to find **i**: **Ans: 500 mA**



$$50 = i * 100$$

$$i = \frac{50}{100} = 500 \text{ mA}$$

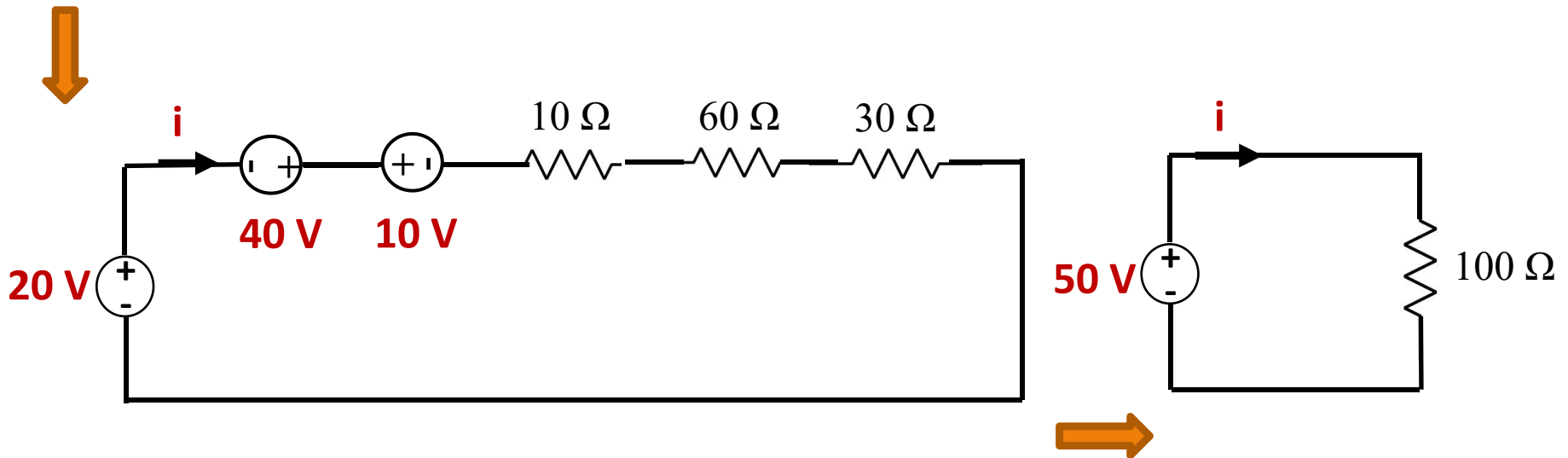


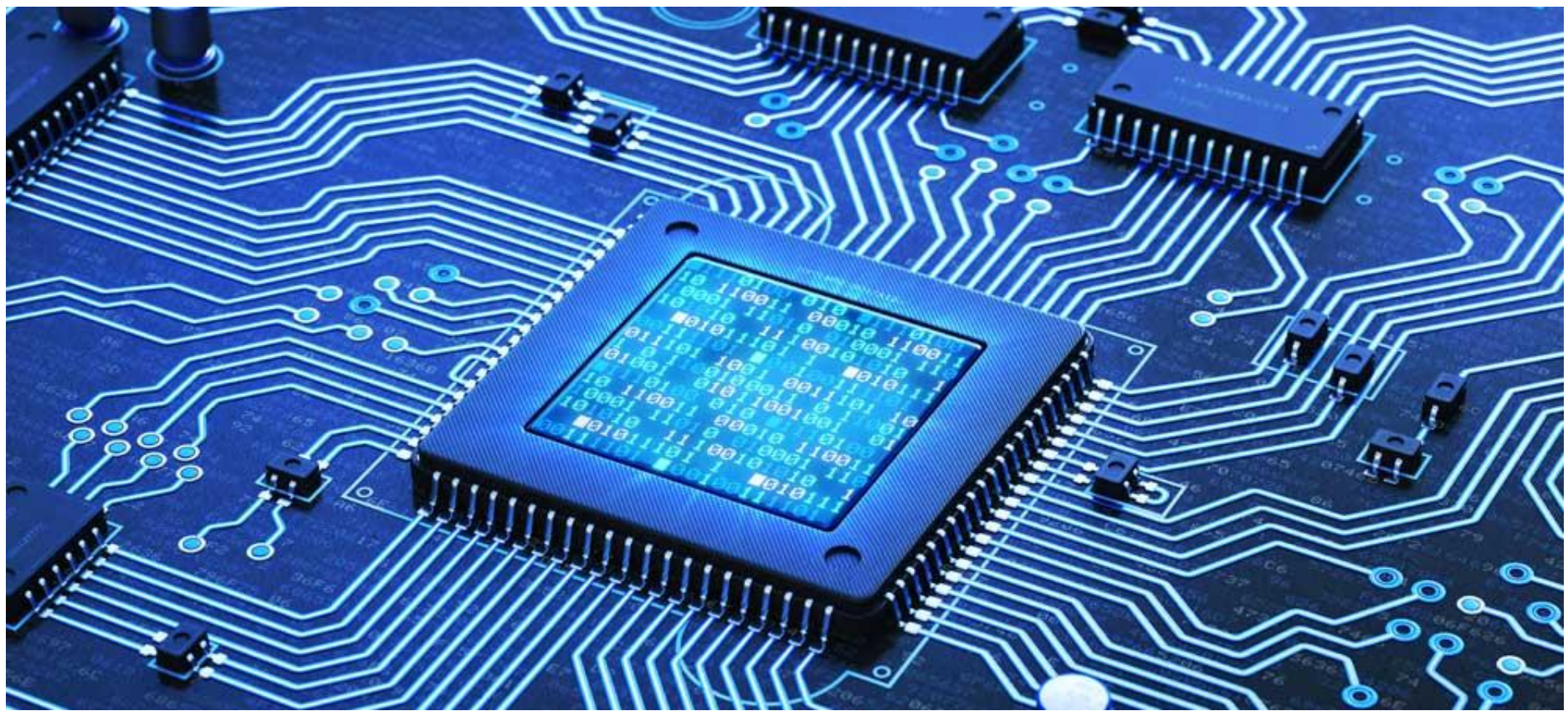

# Resistors in Parallel



# Resistors in Parallel

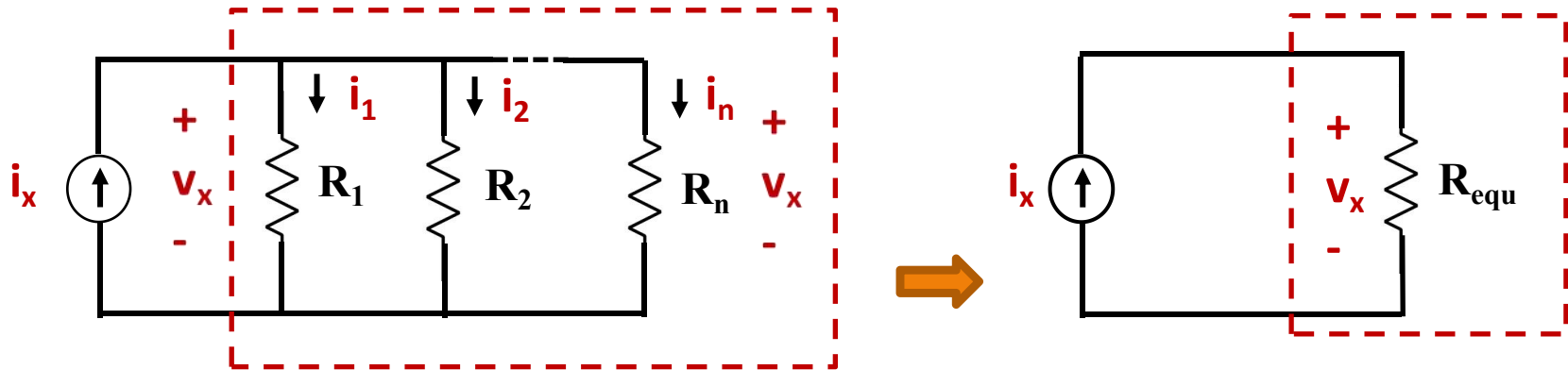

- The voltage ( $v_x$ ) across all the resistors in parallel is the same.
- Applying **KCL** we get:

- $i_x = i_1 + i_2 + \dots + i_n$

- Using Ohm's law:

- $i_x = \frac{v_x}{R_1} + \frac{v_x}{R_2} + \dots + \frac{v_x}{R_n} = v_x \left( \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \right)$

- $i_x = \frac{v_x}{R_{equ}}$

$$\frac{1}{R_{equ}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

# Resistors in Parallel

$$\frac{1}{R_{equ}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

- The  $R_{equ}$  can be written as well:

$$R_{equ}^{-1} = R_1^{-1} + R_2^{-1} + \dots + R_n^{-1}$$

- In terms of **Conductance**:

$$G_{equ} = G_1 + G_2 + \dots + G_n$$

- A parallel combination is also indicated by the following shorthand notation:

$$R_{equ} = R_1 \parallel R_2 \parallel \dots \parallel R_n$$

## Conductance (G)

**Conductance** is the

reciprocal of Resistance =  $\frac{1}{\text{Resistance}}$

$$G = \frac{1}{R}$$

**Unit of Conductance is mho ( $\Omega$ )**

## Two Resistors in Parallel

- The special case of only two parallel resistors is encountered fairly often, and is given by

$$R_{\text{equ}} = R_1 \parallel R_2 \quad \Rightarrow \quad R_{\text{equ}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

- Or, more simply,



$$R_{\text{equ}} = \frac{R_1 R_2}{R_1 + R_2}$$

- The above equation is worth remembering, although it is a common error to attempt to generalize this to more than two resistors, which is incorrect.

$$R_{\text{equ}} \not\equiv \frac{R_1 R_2 R_3}{R_1 + R_2 + R_3}$$

## Problem 5: Resistors in Parallel

- Find  $v$  : **60 V**

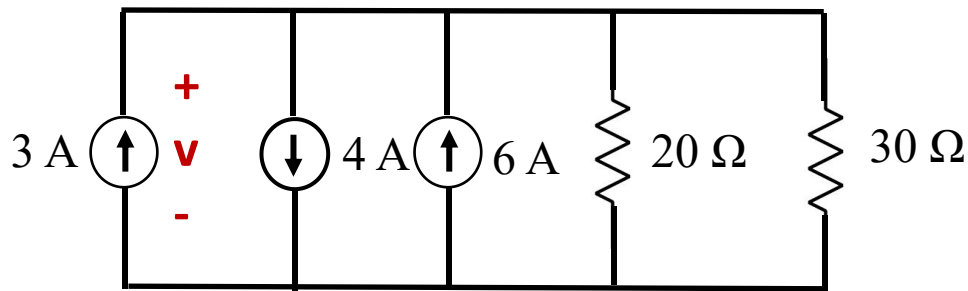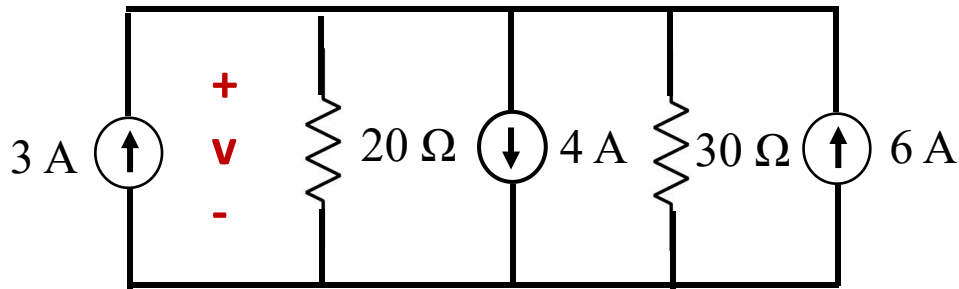

Combine the current sources:


$$i = 3 - 4 + 6 = 5 \text{ A}$$

Combine the parallel resistors:

$$R_{\text{equ}} = \frac{20 * 30}{20 + 30} = 600 / 50$$

$$R_{\text{equ}} = 12 \Omega$$

$$v = 5 * 12 = \mathbf{60 \text{ V}}$$

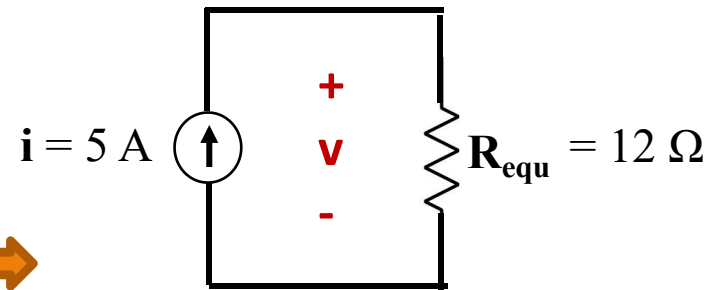



## Session 1.3: Summary

- Conservation of Energy
- Kirchhoff's Current Law
- Kirchhoff's Current Law
- Resistors in Series and Parallel



# Digital Systems and Computer Architecture


## References

# Reference 1: DS & CA

Ref 1

## electronic devices and circuit theory

ROBERT L. BOYLESTAD | LOUIS NASHESKY

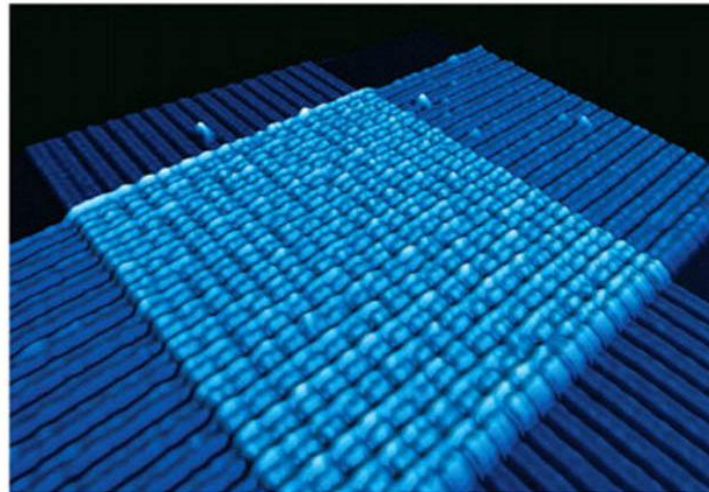



For the  
Module 1



# References 2 & 3: DS & CA

Ref 2

Ref 3

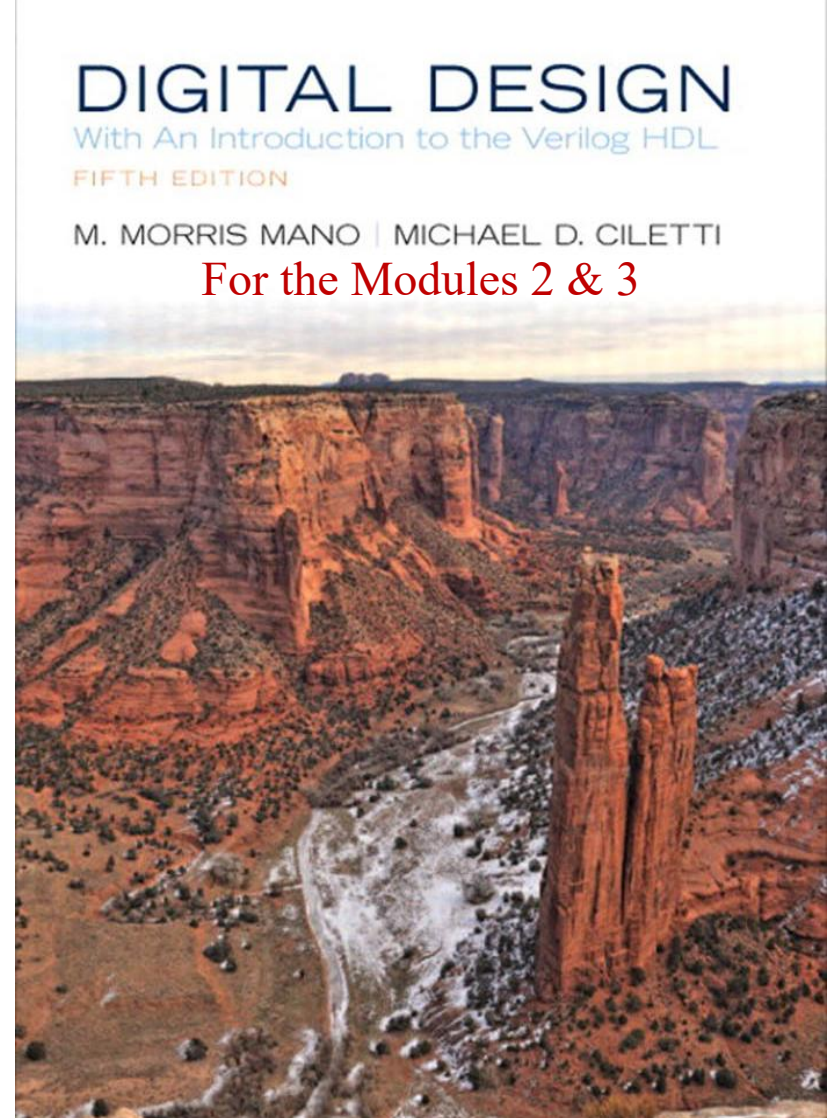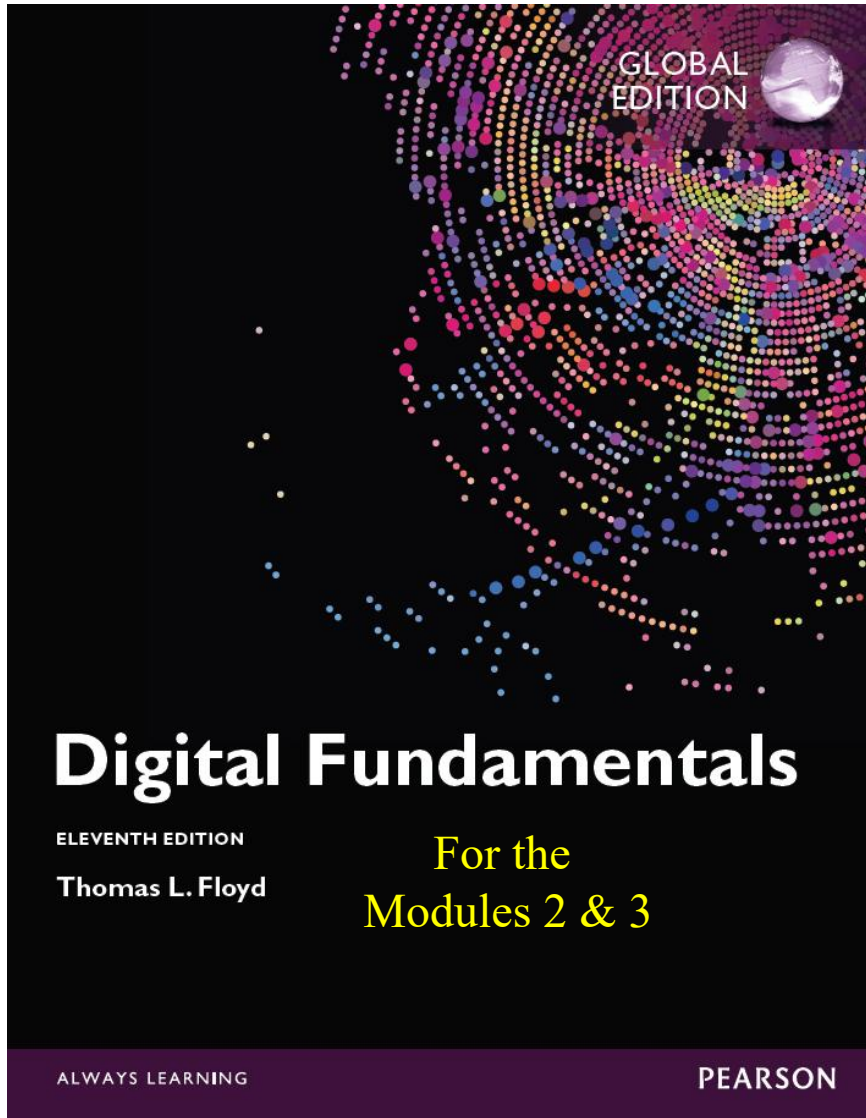




# References 4 & 5: DS and CA

Ref 4

Ref 5

## Digital Design and Computer Architecture

SECOND EDITION

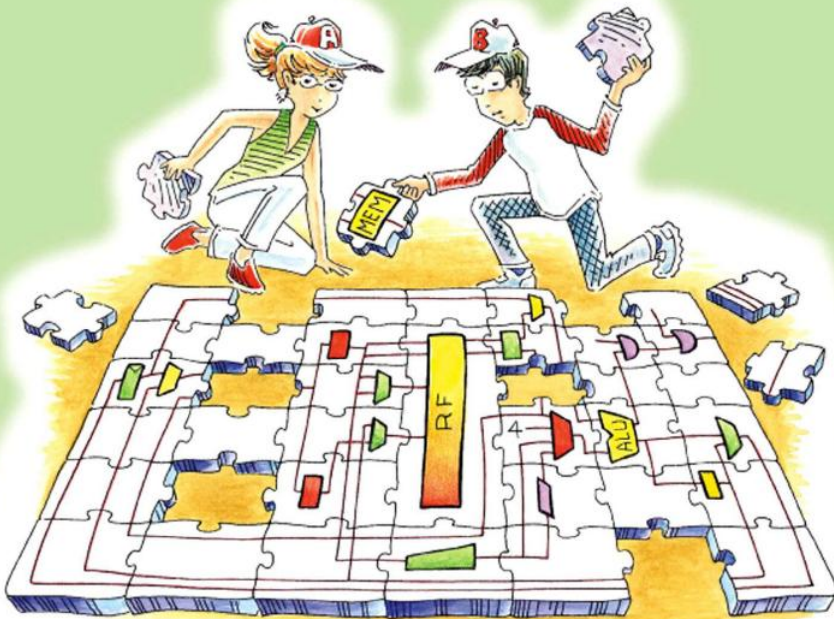

David Money Harris & Sarah L. Harris

MK  
MORGAN KAUFMANN

For the Modules 2 to 5

For the  
Modules 4 & 5



## COMPUTER ORGANIZATION

PRINCIPLES, ANALYSIS, AND DESIGN

LAN JIN • BO HATFIELD